

Digital Logic III

Michael C. Hackett

Assistant Professor, Computer Science



Lecture Topics

- Combinational Circuits
 - Adders
 - Half Adder
 - Full Adder

Adders

- **Adders** are combinational logic circuits capable of performing addition
- A **half adder** has two inputs (the two digits to add) and two outputs (the sum and the carry).

| | | | |
|------------|------------|----------------------|-----------------------------|
| 0 | 1 | 0 | 1 $\leftarrow X_0$ |
| <u>+ 0</u> | <u>+ 0</u> | <u>+ 1</u> | <u>+ 1</u> $\leftarrow X_1$ |
| 00 | 01 | 01 | 10 |
| | | C (<i>Carry</i>) | S (<i>Sum</i>) |

Half Adders

- Half adder truth table:

| X_1 | X_0 | C | S |
|-------|-------|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

$$\begin{array}{r} 0 \\ + 0 \\ \hline 00 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 01 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 01 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$$

X_0 points to the top digit of the last column.
 X_1 points to the bottom digit of the last column.
 C (Carry) points to the left digit of the last column.
 S (Sum) points to the right digit of the last column.

Half Adders

SOP Expressions:


$$C = X_1X_0$$

$$S = \overline{X_1}X_0 + X_1\overline{X_0} = X_1 \oplus X_0$$

| X_1 | X_0 | C | S |
|-------|-------|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |





Half Adders

Half Adder Logic Circuit:

 

Half Adders

Half Adder Logic Circuit:

  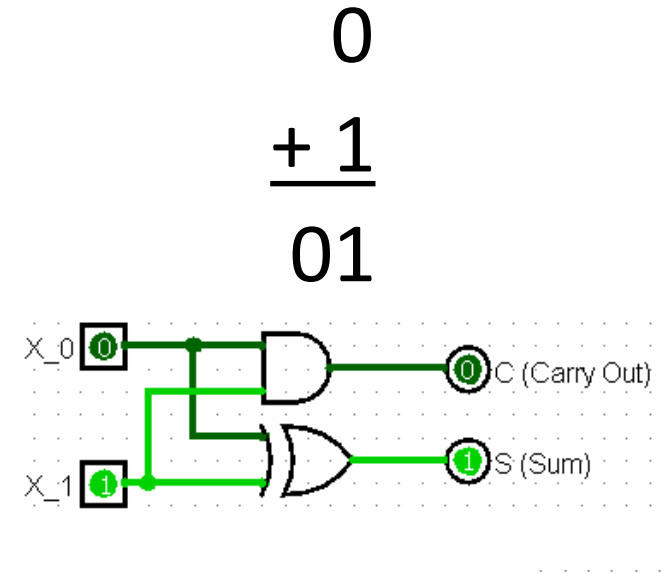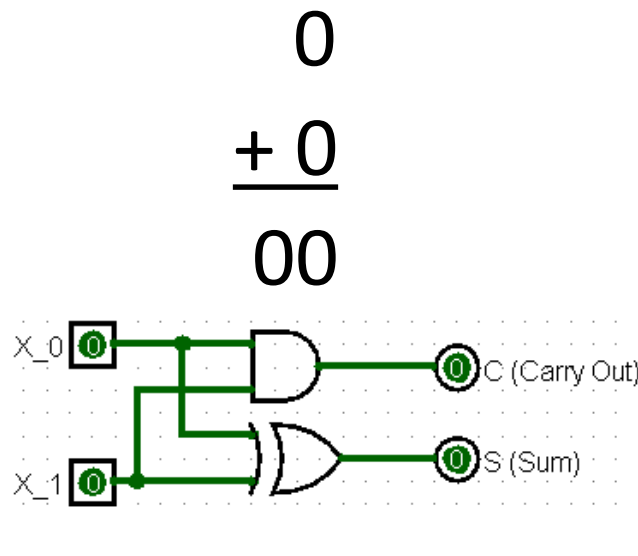

Full Adders

- A **full adder** has three inputs (the two digits to add, plus a value *carried in*) and two outputs (the sum and the carry).

The diagram shows a truth table for a full adder. The inputs are labeled as C_{IN} (Carry In), X_1 , and X_0 . The outputs are labeled as C_{OUT} (Carry Out) and S (Sum). Blue arrows point from the labels to the corresponding values in the equations. The equations are arranged in a column, showing the sum of the three inputs for each combination of X_1 and X_0 .

| C_{IN} | X_1 | X_0 | C_{OUT} | S |
|----------|-------|-------|-----------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adders

- Full adder truth table:

| C_{IN} | X_1 | X_0 | C_{OUT} | S |
|----------|-------|-------|-----------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adders

SOP Expressions:

$$C_{OUT} = \overline{C_{IN}}X_1X_0 + C_{IN}\overline{X_1}X_0 + C_{IN}X_1\overline{X_0} + C_{IN}X_1X_0$$

$$S = \overline{C_{IN}}\overline{X_1}X_0 + \overline{C_{IN}}X_1\overline{X_0} + C_{IN}\overline{X_1}\overline{X_0} + C_{IN}X_1X_0$$

| C_{IN} | X_1 | X_0 | C_{OUT} | S |
|----------|-------|-------|-----------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adders

Simplifying:

$$C_{OUT} = \overline{C_{IN}}X_1X_0 + C_{IN}\overline{X_1}X_0 + C_{IN}X_1\overline{X_0} + \mathbf{C_{IN}X_1X_0}$$

$$C_{OUT} = \mathbf{X_1X_0}(\overline{C_{IN}} + \mathbf{C_{IN}}) + C_{IN}\overline{X_1}X_0 + C_{IN}X_1\overline{X_0}$$

$$C_{OUT} = \mathbf{X_1X_0(1)} + C_{IN}\overline{X_1}X_0 + C_{IN}X_1\overline{X_0}$$

$$C_{OUT} = X_1X_0 + \mathbf{C_{IN}\overline{X_1}X_0} + \mathbf{C_{IN}X_1\overline{X_0}}$$

$$C_{OUT} = X_1X_0 + C_{IN}(\overline{X_1}X_0 + X_1\overline{X_0})$$

$$C_{OUT} = X_1X_0 + C_{IN}(X_0 \oplus X_1)$$

Full Adders

Simplifying:

$$S = \underbrace{\overline{C_{IN}} \overline{X_1} X_0 + \overline{C_{IN}} X_1 \overline{X_0}}_{\text{XOR}} + \underbrace{C_{IN} \overline{X_1} \overline{X_0} + C_{IN} X_1 X_0}_{\text{AND}}$$


$$S = \overline{C_{IN}} (X_0 \oplus X_1) + C_{IN} (X_0 \odot X_1)$$

$$S = \underbrace{\overline{C_{IN}} (X_0 \oplus X_1) + C_{IN} (\overline{X_0 \oplus X_1})}_{\text{XOR}} \quad \bar{X}Y + X\bar{Y} = X \oplus Y$$

$$S = C_{IN} \oplus (X_0 \oplus X_1) = C_{IN} \oplus X_0 \oplus X_1$$

Full Adders




Full Adder Logic Circuit:

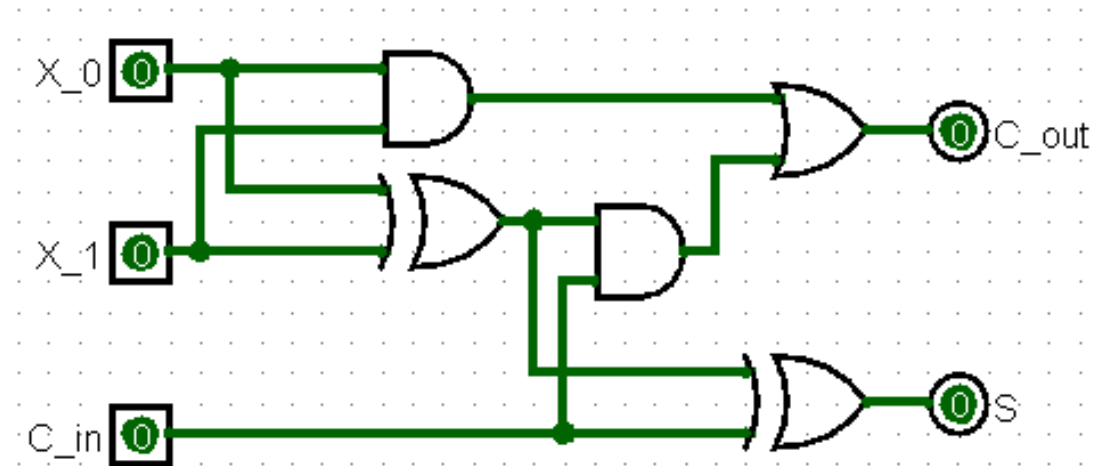

Full Adders


Full Adder Logic Circuit:

| C_{IN} | X_1 | X_0 | C_{OUT} | S |
|----------|-------|-------|-----------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

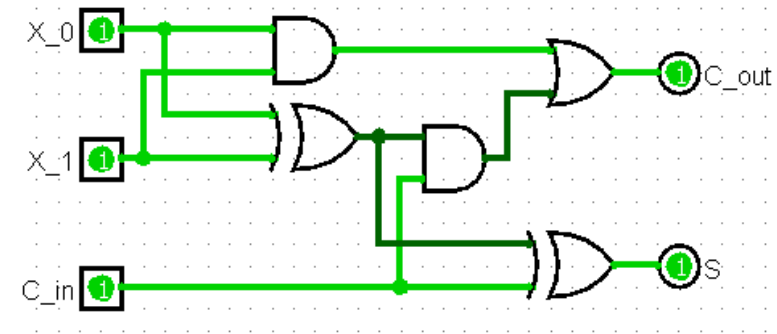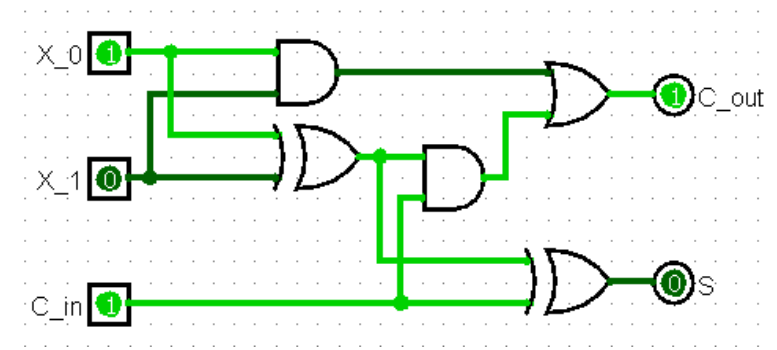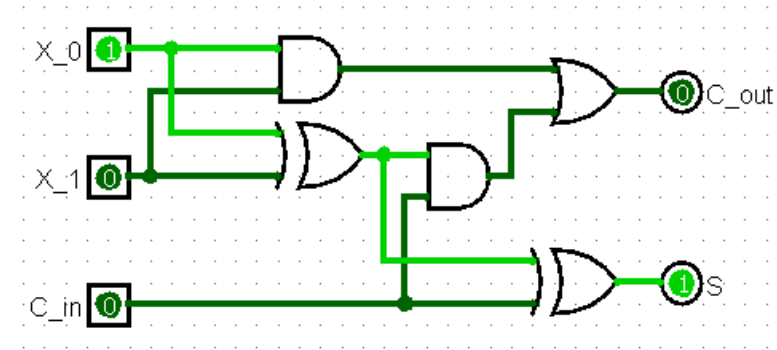

Full Adders




- Abstracted Full Adder:

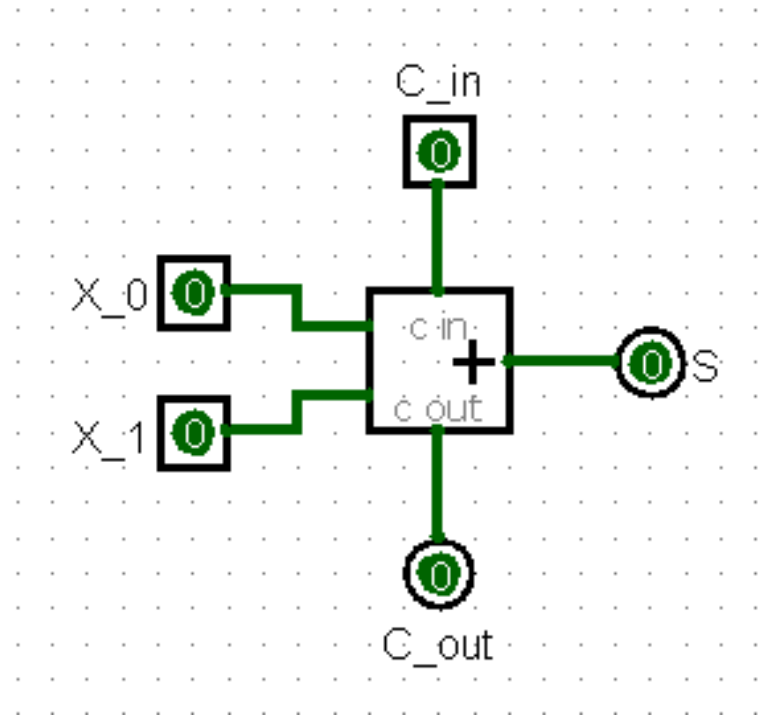

Full Adders

- Abstracted Full Adder:

| C_{IN} | X_1 | X_0 | C_{OUT} | S |
|----------|-------|-------|-----------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

 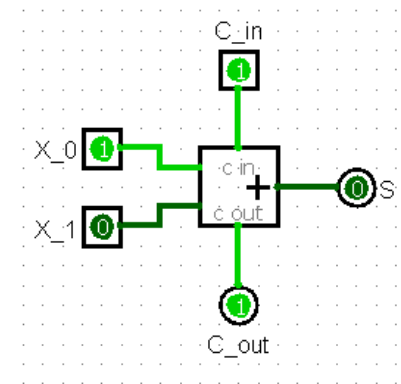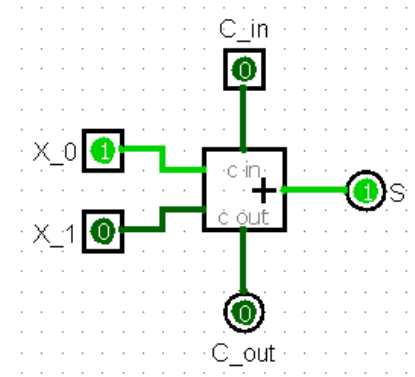


Full Adders

- So far, we've seen only how adders can add single digits together
 - $1+1+1$ or $0+1$ or $1+0+1$ is no problem
 - What if we wanted to add $10+11$ or $11101+10101$?
- Full adders can work together by providing the carry out of one full adder as the carry in for a second adder
 - The technique shown next is a *ripple-carry adder*

$$\begin{array}{r} 001 \\ + 011 \\ \hline 100 \end{array}$$

Full Adders


- For example:

 

Ripple-Carry Adders

- A 2-bit Adder:

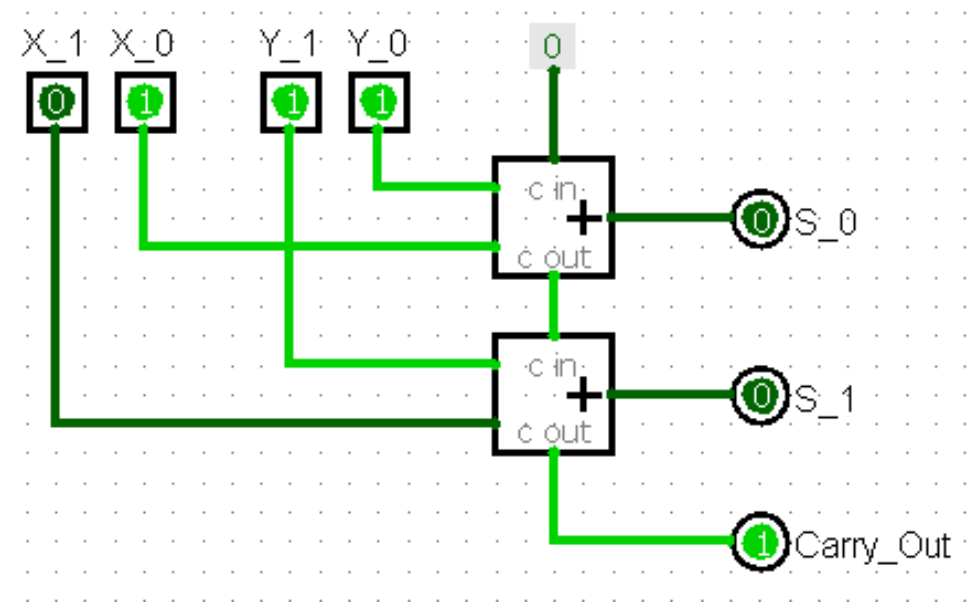
$$\begin{array}{r} 01 \\ + 11 \\ \hline 100 \end{array}$$



Ripple-Carry Adders

- Another example:

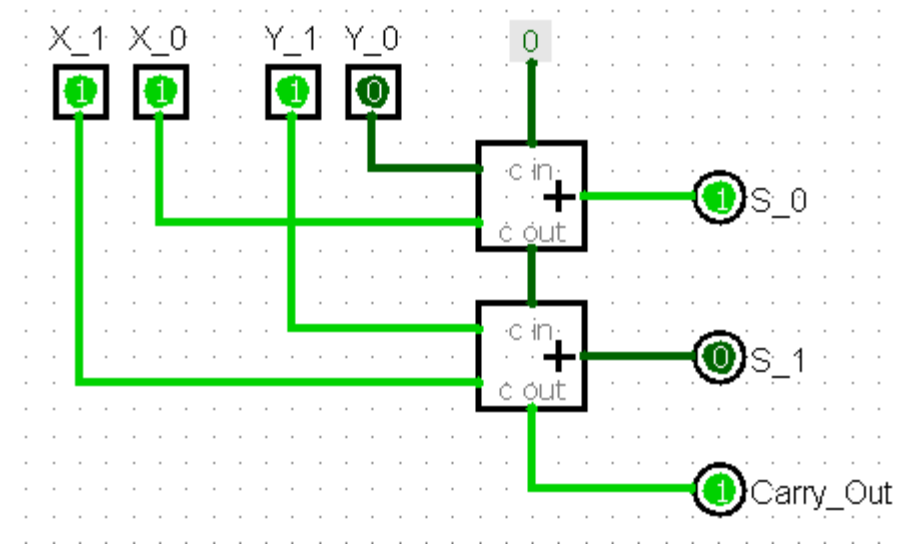
$$\begin{array}{r} 1 1 \\ + 1 0 \\ \hline 1 0 1 \end{array}$$



Ripple-Carry Adders

- A 3-bit Adder:

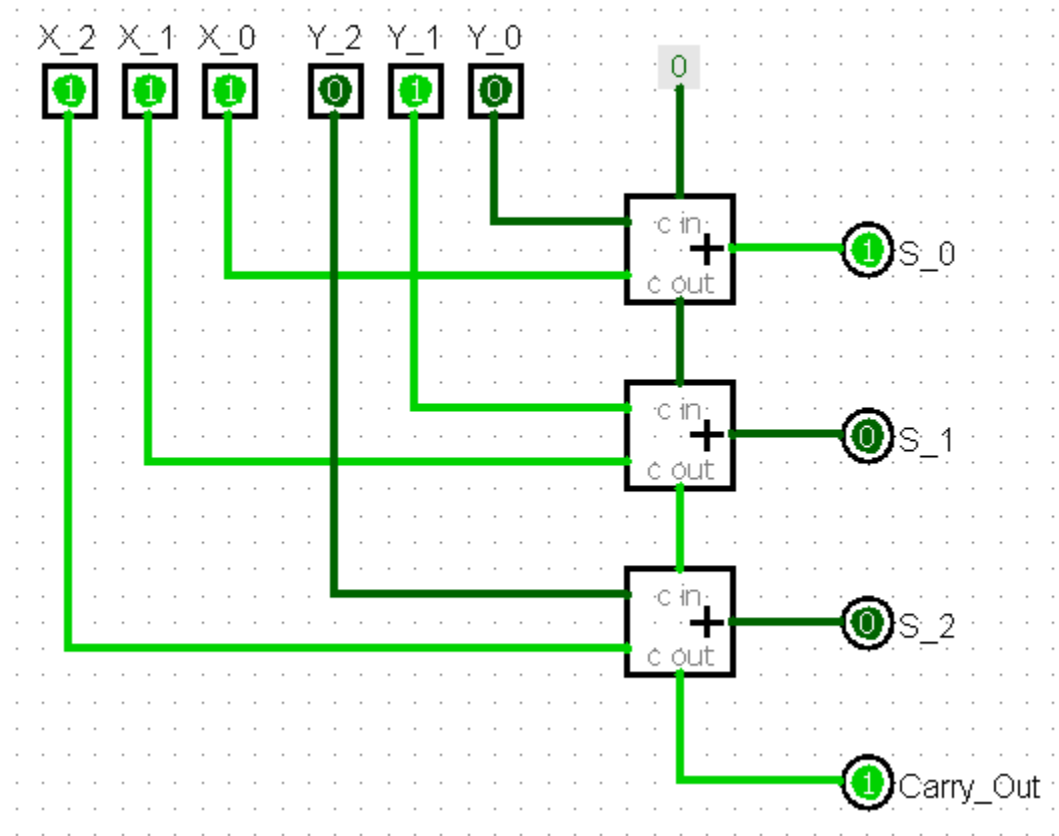
$$\begin{array}{r} \\ \\ + \\ \hline 1 \end{array}$$



Ripple-Carry Adders

- Another example:

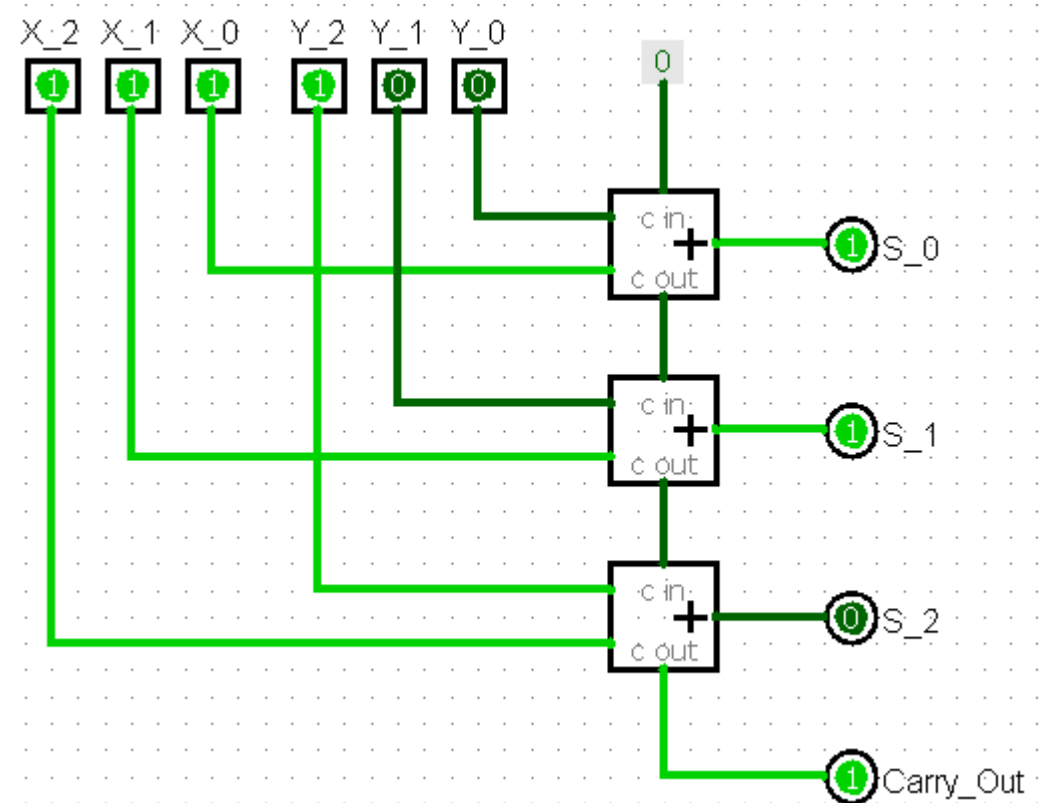
$$\begin{array}{r} \\ \\ + \\ \hline 1 \end{array}$$



Ripple-Carry Adders

- Another example:

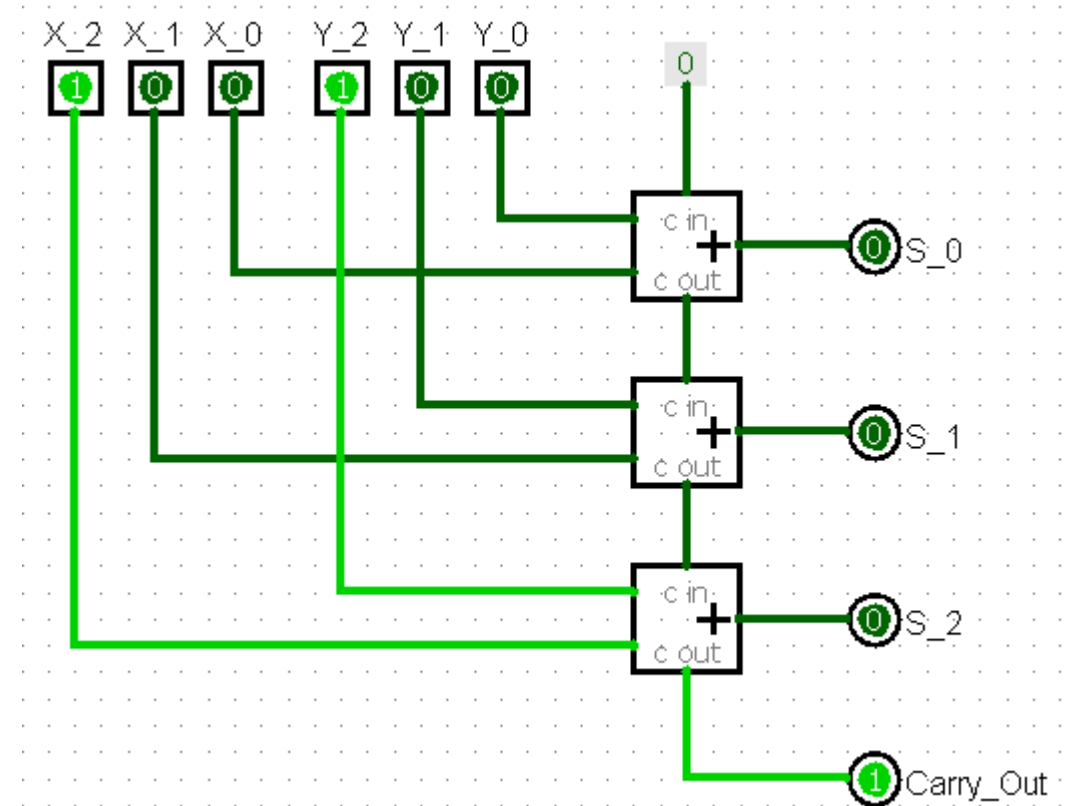
$$\begin{array}{r} 100 \\ + 100 \\ \hline 1000 \end{array}$$



Ripple-Carry Adders

- A 4-bit Adder (with buses):
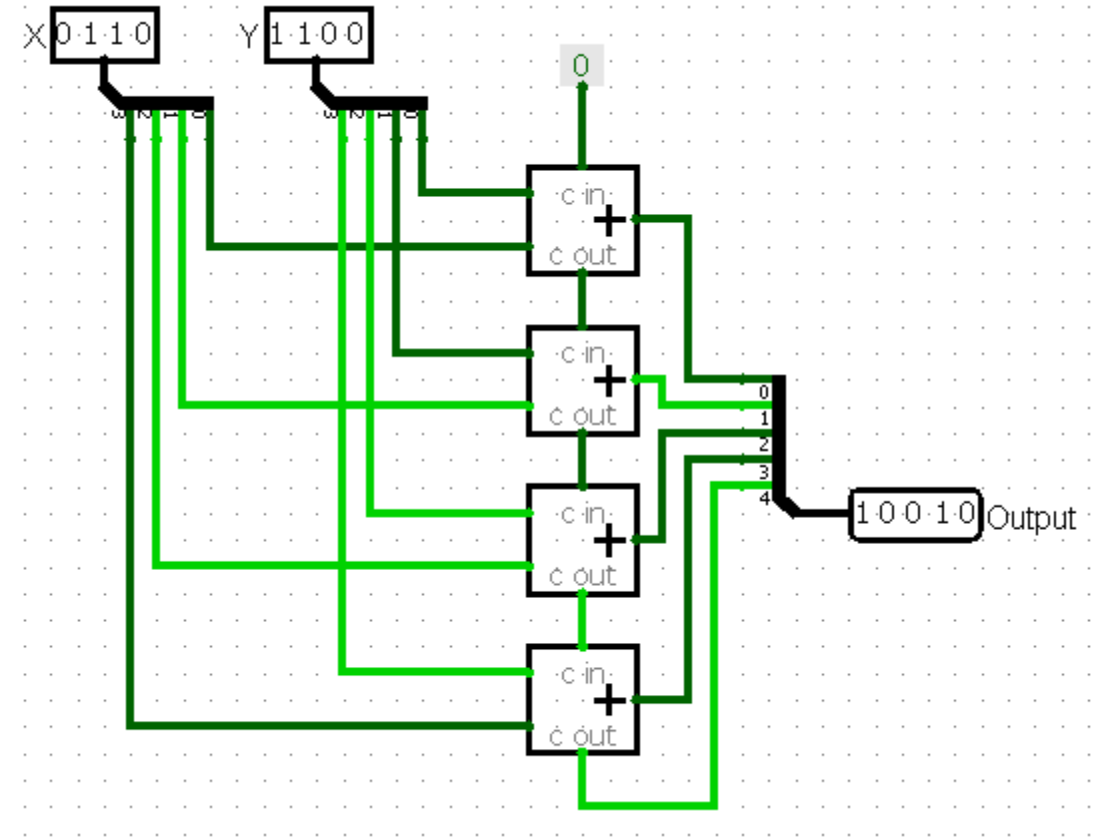
$$\begin{array}{r} 0110 \\ + 1100 \\ \hline 10010 \end{array}$$



Ripple-Carry Adders

- Another example

$$\begin{array}{r} 1010 \\ + 1101 \\ \hline 10111 \end{array}$$

