

Digital Logic I

Michael C. Hackett

Assistant Professor, Computer Science

Lecture Topics

- Boolean Functions
- Boolean Expressions
- Simplifying Boolean Expressions
 - Karnaugh Maps
- Logic Gates and Circuits
- Buses
- Sign Extends

Boolean Functions

- We've become familiar with logical operations (and, or, not...) while working with and assembly language (and high-level languages in other courses)
- With more complex logical expressions, we use special notations to represent Boolean functions.
 - Some of these notations were seen in a previous lecture

Boolean Functions

$x \text{ AND } y$

may be expressed as either:

$x \cdot y$

xy

| x | y | $x \text{ AND } y$ |
|-----|-----|--------------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Boolean Functions

$x \text{ OR } y$
is expressed as:

$$x + y$$

| x | y | $x \text{ OR } y$ |
|-----|-----|-------------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

Boolean Functions

NOT x

may be expressed as either:

x' ("*x prime*")

\overline{x} ("*x bar*" or "*not x*")

| x | <i>NOT x</i> |
|-----|--------------|
| 0 | 1 |
| 1 | 0 |

Boolean Functions

$x \text{ XOR } y$
is expressed as:

$$\bar{x}y + x\bar{y}$$
$$x \oplus y$$

| x | y | $x \text{ XOR } y$ |
|-----|-----|--------------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Boolean Functions

- An **NOR** operation results in true (1) only when **both** of the operands are false (0)
 - It is the negation of the **or** operator

$x \text{ NOR } y$

is expressed as:

$$\overline{x + y}$$

| x | y | $x \text{ NOR } y$ |
|-----|-----|--------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Boolean Functions

- A **NAND** operation results in true (1) only when **both** of the operands are *not* true (1)
 - It is the negation of the **and** operator

$x \text{ NAND } y$

may be expressed as either:

$$\overline{x \cdot y}$$

$$\overline{xy}$$

| x | y | $x \text{ NAND } y$ |
|-----|-----|---------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Boolean Functions

- An **XNOR** (exclusive **nor**, “*x nor*”; “*znor*”) operation results in true (1) only when the operands are either both true (1) or both false (0)
 - It is the negation of the **xor** operator

$x \text{ XNOR } y$

is expressed as:

$$\bar{x} \bar{y} + xy$$

$$x \odot y$$

| x | y | $x \text{ XNOR } y$ |
|-----|-----|---------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Boolean Functions

- The precedence for Boolean operators is
 1. *Expressions in parentheses*
 2. *NOT*
 3. *AND*
 4. *OR*
- $x \text{ NOR } y = \text{NOT}(x \text{ OR } y)$
- $x \text{ NAND } y = \text{NOT}(x \text{ AND } y)$
- $x \text{ XNOR } y = \text{NOT}(x \text{ XOR } y)$
- $x \text{ XOR } y = (\text{NOT}(x) \text{ AND } y) \text{ OR } (x \text{ AND } \text{NOT}(y))$

Boolean Expressions

- Boolean expressions can be evaluated using truth tables
 - Be sure to follow the order of operations

$$\overline{x} + y$$

| | | 1 | 2 |
|-----|-----|----------------|--------------------|
| x | y | \overline{x} | $\overline{x} + y$ |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 |

Boolean Expressions

- Boolean expressions can be evaluated using truth tables

$$x + xy$$

| | | 1 | 2 |
|-----|-----|------|----------|
| x | y | xy | $x + xy$ |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Boolean Expressions

- Boolean expressions can be evaluated using truth tables

$$\bar{x} + xy + \bar{y}$$

| | | 1 | 2 | 3 | 4 | 5 |
|-----|-----|-----------|-----------|------|----------------|--------------------------|
| x | y | \bar{x} | \bar{y} | xy | $\bar{x} + xy$ | $\bar{x} + xy + \bar{y}$ |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 |

- This truth table tells us that, regardless of the value of x or y, the result will always be 1

Boolean Expressions

- Boolean expressions can be evaluated using truth tables

$$x + y\bar{z}$$

| | | | 1 | 2 | 3 |
|-----|-----|-----|-----------|------------|----------------|
| x | y | z | \bar{z} | $y\bar{z}$ | $x + y\bar{z}$ |
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 |

Boolean Expressions


- We'll take the previous expressions and convert them to **sum-of-products form** (or, *disjunctive normal form*)
- This form can be obtained with a truth table
- We are interested in the scenarios where the output of the function is 1 (true)

Boolean Expressions

- Converting to Sum-of-Products

$$\bar{x} + y$$

| x | y | \bar{x} | $\bar{x} + y$ |
|-----|-----|-----------|---------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 |
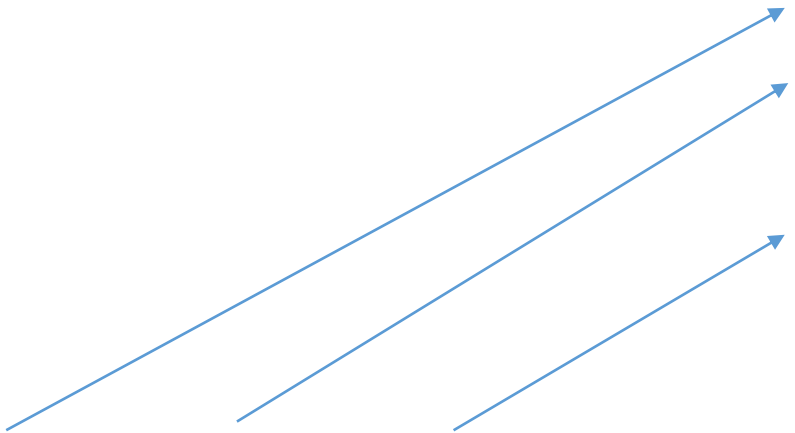
$$\bar{x}\bar{y} + \bar{x}y + xy$$


Boolean Expressions

- Proving their identity

$$\bar{x} + y = \bar{x}\bar{y} + \bar{x}y + xy$$

| Original | | | | | SOP Form | | | |
|----------|-----|-----------|-----------|---------------|------------------|------------|------|----------------------------------|
| x | y | \bar{x} | \bar{y} | $\bar{x} + y$ | $\bar{x}\bar{y}$ | $\bar{x}y$ | xy | $\bar{x}\bar{y} + \bar{x}y + xy$ |
| 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 |

Boolean Expressions

- Converting to Sum-of-Products

$$x + xy$$

| x | y | xy | $x + xy$ |
|-----|-----|------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$$x\bar{y} + xy$$


Boolean Expressions

- Converting to Sum-of-Products

$$\bar{x} + xy + \bar{y}$$

| x | y | \bar{x} | \bar{y} | xy | $\bar{x} + xy$ | $\bar{x} + xy + \bar{y}$ |
|-----|-----|-----------|-----------|------|----------------|--------------------------|
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 |


$$\bar{x}\bar{y} + \bar{x}y + x\bar{y} + xy$$


Boolean Expressions

- Converting to Sum-of-Products

$$x + y\bar{z}$$

| x | y | z | \bar{z} | $y\bar{z}$ | $x + y\bar{z}$ |
|----------|----------|----------|-----------|------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 |
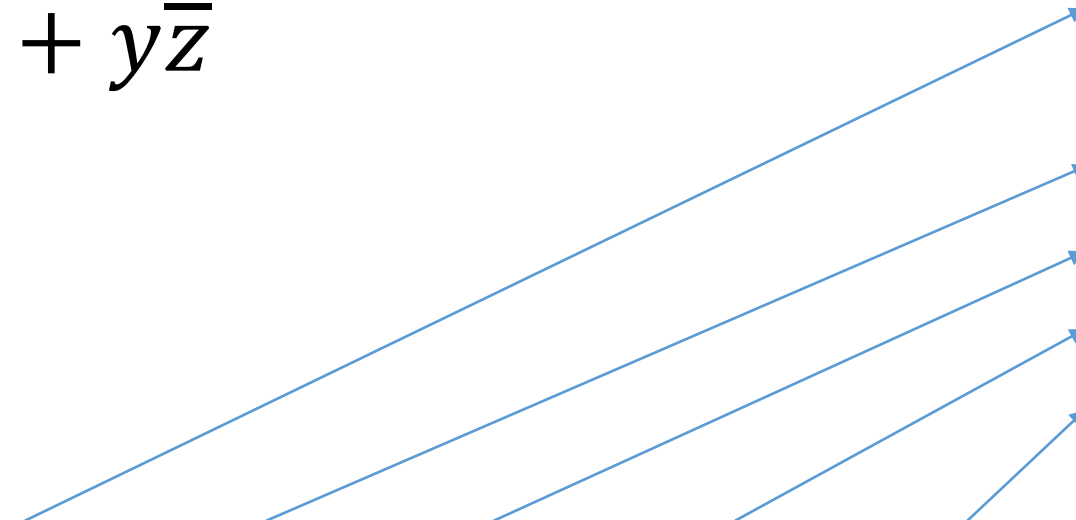
$$\bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z + xy\bar{z} + xyz$$


Boolean Expressions

- We are now ready to look at some laws of Boolean algebra that will let us simplify Boolean expressions to the fewest terms and operations needed.

$$\bar{x} + y = \bar{x}\bar{y} + \bar{x}y + xy$$

- Though these expressions are logically equivalent, the first expression uses fewer terms and operations than the second.

Boolean Expressions

- Identity Laws

$$x \cdot 1 = x$$

$$x + 0 = x$$

| x | $x \cdot 1$ | $x + 0$ |
|----------|-------------|----------|
| 0 | 0 | 0 |
| 1 | 1 | 1 |

Boolean Expressions

- Constant Laws

$$x \cdot 0 = 0$$

$$x + 1 = 1$$

| x | $x \cdot 0$ | $x + 1$ |
|-----|-------------|----------|
| 0 | 0 | 1 |
| 1 | 0 | 1 |

Boolean Expressions

- Negation Laws

$$x \cdot \bar{x} = 0$$

$$x + \bar{x} = 1$$

| x | \bar{x} | $x \cdot \bar{x}$ | $x + \bar{x}$ |
|-----|-----------|-------------------|---------------|
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |

Boolean Expressions

- Double Negation Law

$$\overline{\overline{x}} = x$$

| x | \overline{x} | $\overline{\overline{x}}$ |
|-----|----------------|---------------------------|
| 0 | 1 | 0 |
| 1 | 0 | 1 |

Boolean Expressions

- Idempotent Laws

$$x \cdot x = x$$

$$x + x = x$$

| x | $x \cdot x$ | $x + x$ |
|-----|-------------|---------|
| 0 | 0 | 0 |
| 1 | 1 | 1 |

Boolean Expressions

- Commutative Laws

$$x \cdot y = y \cdot x$$

$$x + y = y + x$$

| x | y | $x \cdot y$ | $y \cdot x$ |
|-----|-----|-------------|-------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 |

| x | y | $x + y$ | $y + x$ |
|-----|-----|---------|---------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 |

Boolean Expressions

- Distributive Laws

$$x \cdot (y + z) = xy + xz$$

| x | y | z | $(y + z)$ | $x \cdot (y + z)$ |
|-----|-----|-----|-----------|-------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| x | y | z | xy | xz | $xy + xz$ |
|-----|-----|-----|------|------|-----------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 |

Boolean Expressions

- Distributive Laws

$$x + (yz) = (x + y) \cdot (x + z)$$

| x | y | z | (yz) | $x + (yz)$ |
|-----|-----|-----|--------|------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| x | y | z | $(x + y)$ | $(x + z)$ | $(x + y) \cdot (x + z)$ |
|-----|-----|-----|-----------|-----------|-------------------------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 |

Boolean Expressions

- Associative Laws

$$x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

| x | y | z | $(y \cdot z)$ | $x \cdot (y \cdot z)$ |
|-----|-----|-----|---------------|-----------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

| x | y | z | $(x \cdot y)$ | $(x \cdot y) \cdot z$ |
|-----|-----|-----|---------------|-----------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Boolean Expressions

- Associative Laws

$$x + (y + z) = (x + y) + z$$

| x | y | z | $(y + z)$ | $x + (y + z)$ |
|-----|-----|-----|-----------|---------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| x | y | z | $(x + y)$ | $(x + y) + z$ |
|-----|-----|-----|-----------|---------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Boolean Expressions

- DeMorgan's Laws

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$

| x | y | $x + y$ | $\overline{x + y}$ |
|-----|-----|---------|--------------------|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 |

| x | y | \bar{x} | \bar{y} | $\bar{x} \cdot \bar{y}$ |
|-----|-----|-----------|-----------|-------------------------|
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |

Boolean Expressions

- DeMorgan's Laws

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

| x | y | $x \cdot y$ | $\overline{x \cdot y}$ |
|-----|-----|-------------|------------------------|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

| x | y | \bar{x} | \bar{y} | $\bar{x} + \bar{y}$ |
|-----|-----|-----------|-----------|---------------------|
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |

Boolean Expressions

- Absorption Laws

$$x + (x \cdot y) = x$$

$$x \cdot (x + y) = x$$

| x | y | $x \cdot y$ | $x + (x \cdot y)$ |
|-----|-----|-------------|-------------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 |

| x | y | $x + y$ | $x \cdot (x + y)$ |
|-----|-----|---------|-------------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 |

Boolean Expressions

- Absorption Laws

$$x + (\bar{x} \cdot y) = x + y$$

$$x \cdot (\bar{x} + y) = x \cdot y$$

| x | y | \bar{x} | $x + y$ | $\bar{x} \cdot y$ | $x + (\bar{x} \cdot y)$ |
|-----|-----|-----------|---------|-------------------|-------------------------|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 |

| x | y | \bar{x} | $x \cdot y$ | $\bar{x} + y$ | $x \cdot (\bar{x} + y)$ |
|-----|-----|-----------|-------------|---------------|-------------------------|
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 |

Boolean Expressions

- Consensus Laws

$$xy + \bar{x}z + yz = xy + \bar{x}z$$

| x | y | z | \bar{x} | xy | $\bar{x}z$ | yz | $xy + \bar{x}z$ | $xy + \bar{x}z + yz$ |
|-----|-----|-----|-----------|------|------------|------|-----------------|----------------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 |

Boolean Expressions

- Consensus Laws

$$(x + y) \cdot (\bar{x} + z) \cdot (y + z) = (x + y) \cdot (\bar{x} + z)$$

| x | y | z | \bar{x} | $x + y$ | $\bar{x} + z$ | $y + z$ | $(x + y) \cdot (\bar{x} + z)$ | $(x + y) \cdot (\bar{x} + z) \cdot (y + z)$ |
|-----|-----|-----|-----------|---------|---------------|---------|-------------------------------|---|
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |

Boolean Expressions

- An earlier example:

$$\bar{x} + y = \bar{x}\bar{y} + \bar{x}y + xy$$

- Let's use any applicable laws to the SOP expression:

$$\bar{x}\bar{y} + \bar{x}y + xy$$

- To arrive at its equivalent:

$$\bar{x} + y$$

Boolean Expressions

- Distributive Law:
 $x \cdot (y + z) = \mathbf{xy} + \mathbf{xz}$

$$\bar{x}\bar{y} + \bar{x}y + xy$$

$$\bar{\mathbf{x}}\bar{\mathbf{y}} + \bar{\mathbf{x}}\mathbf{y} + \mathbf{xy}$$

- Negation Law:
 $\mathbf{x} + \bar{\mathbf{x}} = 1$

$$\bar{x}(\bar{y} + y) + xy$$

$$\bar{x}(\bar{\mathbf{y}} + \mathbf{y}) + \mathbf{xy}$$

- Identity Law:
 $\mathbf{x} \cdot \mathbf{1} = \mathbf{x}$

$$\bar{x}(1) + xy$$

$$\bar{\mathbf{x}}(\mathbf{1}) + \mathbf{xy}$$

- Absorption Law:
 $\mathbf{x} + (\bar{\mathbf{x}} \cdot \mathbf{y}) = \mathbf{x} + \mathbf{y}$

$$\bar{x} + xy$$

$$\bar{\mathbf{x}} + \mathbf{xy}$$

$$\bar{x} + y$$

Boolean Expressions

- An earlier example:

$$x + xy = x\bar{y} + xy$$

was proven to be true with a truth table

- Let's use any applicable laws to this SOP expression to see if the Boolean expression can be simplified further:

$$x\bar{y} + xy$$

Boolean Expressions

Distributive Law:

$$x \cdot (y + z) = \mathbf{xy} + \mathbf{xz}$$

$$x\bar{y} + xy$$

$$\mathbf{x\bar{y}} + \mathbf{xy}$$

- Negation Law:

$$\mathbf{x} + \bar{\mathbf{x}} = 1$$

$$x(\bar{y} + y)$$

$$x(\bar{\mathbf{y}} + \mathbf{y})$$

- Identity Law:

$$\mathbf{x} \cdot \mathbf{1} = x$$

$$x(1)$$

$$\mathbf{x(1)}$$

$$x$$

Boolean Expressions

$$x + xy = x\bar{y} + xy = x$$

| x | y | \bar{y} | xy | $x\bar{y}$ | $x + xy$ | $x\bar{y} + xy$ |
|-----|-----|-----------|------|------------|----------|-----------------|
| 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 |

Boolean Expressions

- An earlier example:

$$\bar{x} + xy + \bar{y} = \bar{x}\bar{y} + \bar{x}y + x\bar{y} + xy$$

- We not only proved this to be true with truth tables, but we also saw the result is always 1

| x | y | \bar{x} | \bar{y} | xy | $\bar{x} + xy$ | $\bar{x} + xy + \bar{y}$ |
|-----|-----|-----------|-----------|------|----------------|--------------------------|
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 |

- Let's also prove it true using any applicable laws

Boolean Expressions

| | | | |
|--|---|-------------|--|
| <ul style="list-style-type: none"> Distributive Law: $x \cdot (y + z) = xy + xz$ Negation Law: $x + \bar{x} = 1$ Identity Law: $x \cdot 1 = x$ | $\bar{x}\bar{y} + \bar{x}y + x\bar{y} + xy$ $\bar{x}\bar{y} + \bar{x}y + x\bar{y} + xy$ $\bar{x}(\bar{y} + y) + x\bar{y} + xy$ $\bar{x}(\bar{y} + y) + x\bar{y} + xy$ $\bar{x}(1) + x\bar{y} + xy$ $\bar{x}(1) + x\bar{y} + xy$ $\bar{x} + x\bar{y} + xy$ | <div></div> | $\bar{x} + x\bar{y} + xy$ $\bar{x} + x\bar{y} + xy$ $\bar{x} + x(\bar{y} + y)$ $\bar{x} + x(\bar{y} + y)$ $\bar{x} + x(1)$ $\bar{x} + x(1)$ $\bar{x} + x$ $\bar{x} + x$ 1 |
| | | <div></div> | <ul style="list-style-type: none"> Distributive Law: $x \cdot (y + z) = xy + xz$ Negation Law: $x + \bar{x} = 1$ Identity Law: $x \cdot 1 = x$ Negation Law: $x + \bar{x} = 1$ |

Boolean Expressions

- An earlier example:

$$x + y\bar{z} = \bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z + xy\bar{z} + xyz$$

was proven to be true with a truth table

- Let's use any applicable laws to the SOP expression:

$$\bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z + xy\bar{z} + xyz$$

- To arrive at its equivalent:

$$x + y\bar{z}$$

Boolean Expressions

- Distributive Law:

$$\bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z + xy\bar{z} + xyz$$
$$x(\bar{y}\bar{z} + \bar{y}z + y\bar{z} + yz) + \bar{x}y\bar{z}$$

- Distributive Law (x2):

$$x(\bar{y}\bar{z} + \bar{y}z + y\bar{z} + yz) + \bar{x}y\bar{z}$$
$$x(\bar{y}(\bar{z} + z) + y(\bar{z} + z)) + \bar{x}y\bar{z}$$

- Negation Law (x2):

$$x(\bar{y}(\bar{z} + z) + y(\bar{z} + z)) + \bar{x}y\bar{z}$$
$$x(\bar{y}(1) + y(1)) + \bar{x}y\bar{z}$$

- Identity Law (x2):

$$x(\bar{y} + y) + \bar{x}y\bar{z}$$

- Negation Law:

$$x(\bar{y} + y) + \bar{x}y\bar{z}$$
$$x(1) + \bar{x}y\bar{z}$$

- Identity Law:

$$x + \bar{x}y\bar{z}$$

- Absorption Law:

$$x + (\bar{x} \cdot y) = x + y$$

$$x + \bar{x}y\bar{z}$$

$$x + y\bar{z}$$

Simplifying Boolean Expressions

- Those laws are useful for reducing expressions, but it can be cumbersome to reduce very complex expression this way
- A tool used to help with the simplification process is a Karnaugh Map
 - K-Map, for short
- K-Maps are not a total substitute for Boolean algebra, but they are faster

Simplifying Boolean Expressions

- Below is a two-variable K-Map
 - Notice that only one bit changes between each row and column

| | | y | |
|-----|-------------|-----------|-----|
| | | \bar{y} | y |
| x | \bar{x} 0 | 00 | 01 |
| | x 1 | 10 | 11 |

Simplifying Boolean Expressions

- To demonstrate, we'll use the following expression:

$$x + \bar{y}$$

- Which yields the following truth table:

| x | y | \bar{y} | $x + \bar{y}$ |
|-----|-----|-----------|---------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |

Simplifying Boolean Expressions

| x | y | \bar{y} | $x + \bar{y}$ |
|----------|----------|-----------|---------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |

| | | y | |
|-----|-----------|----------------|-----|
| | | \bar{y} | y |
| x | \bar{x} | 0 | 1 |
| | 0 | 1 00 | 01 |
| x | 1 | 10 | 11 |

Simplifying Boolean Expressions

| x | y | \bar{y} | $x + \bar{y}$ |
|----------|----------|-----------|---------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |

| | | y | |
|-----|-----------|-----------|-----------------------|
| | | \bar{y} | y |
| x | \bar{x} | 0 | 1 |
| | 0 | 1 00 | 0 01 |
| x | 1 | 10 | 11 |

Simplifying Boolean Expressions

| x | y | \bar{y} | $x + \bar{y}$ |
|----------|----------|-----------|---------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |

| | | y | |
|-----|-------------|----------------|----------|
| | | \bar{y} 0 | y 1 |
| x | \bar{x} 0 | 1 00 | 0 01 |
| | x 1 | 1 10 | 11 |

Simplifying Boolean Expressions

| x | y | \bar{y} | $x + \bar{y}$ |
|-----|-----|-----------|---------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |

| | | y | |
|-----|-----------|-----------|---------|
| | | \bar{y} | y |
| x | \bar{x} | 0 | 1 |
| | 0 | 1 00 | 0 01 |
| x | 1 | 1 10 | 1 11 |

Simplifying Boolean Expressions

- K-Map for $x + \bar{y}$

| | | <i>y</i> | |
|-----------------|-------------|-----------------|---------|
| | | \bar{y} | y |
| <i>x</i> | \bar{x} 0 | 1 00 | 0 01 |
| | x 1 | 1 10 | 1 11 |

Simplifying Boolean Expressions

- Resulting SOP Expression: $\bar{x} \bar{y} + x\bar{y} + xy$

| | | y | |
|-----|-------------|----------------|----------------|
| | | \bar{y} | y |
| x | \bar{x} 0 | 1 00 | 0 01 |
| | x 1 | 1 10 | 1 11 |

Simplifying Boolean Expressions

- When using K-Maps, we can group adjacent cells together in order to simplify the function

| | | y | |
|-----|-------------|-----------|---------|
| | | \bar{y} | y |
| x | \bar{x} 0 | 1 00 | 0 01 |
| | x 1 | 1 10 | 1 11 |

- This illustrates the output is 1 when $y = 0$ (it does not depend on x)

Simplifying Boolean Expressions

- When grouping adjacent cells, you must group them in powers of 2
 - A group of 2, 4, 8, etc.
- The grouped cells must all contain 1s
- Cells cannot be grouped diagonally

Simplifying Boolean Expressions

| | | y | |
|-----|-------------|-----------|---------|
| | | \bar{y} | y |
| x | \bar{x} 0 | 1 00 | 0 01 |
| | x 1 | 1 10 | 1 11 |

$\bar{y} + xy$

Simplifying Boolean Expressions

- We can reuse 1's that were grouped with other adjacent cells

A Karnaugh map for a 2-variable Boolean function with variables x and y . The map is a 2x2 grid. The columns are labeled \bar{y} (0) and y (1). The rows are labeled \bar{x} (0) and x (1). The cells contain the following values: $\bar{x}\bar{y}$ is 1, $\bar{x}y$ is 0, $x\bar{y}$ is 1, and xy is 1. Two groups of 1s are highlighted with black boxes: a vertical group for $\bar{x}y$ (cells 00 and 10) and a horizontal group for x (cells 10 and 11). The cell 10 is part of both groups.

| | | y | |
|-----|-------------|----------------|----------|
| | | \bar{y} 0 | y 1 |
| x | \bar{x} 0 | 1 00 | 0 01 |
| | x 1 | 1 10 | 1 11 |

- This second grouping illustrates the output is 1 when $x = 1$ (it does not depend on y)

Simplifying Boolean Expressions

| | | y | |
|-----|-------------|-----------|---------|
| | | \bar{y} | y |
| x | \bar{x} 0 | 1 00 | 0 01 |
| | x 1 | 1 10 | 1 11 |

$\bar{y} + x$

- Our original expression was $x + \bar{y}$
 - Already reduced to fewest terms

Simplifying Boolean Expressions

- Here's an SOP Expression from earlier: $\bar{x}\bar{y} + \bar{x}y + x\bar{y} + xy$
 - The one that always results in 1

| | | y | |
|-----|-------------|----------------|----------------|
| | | \bar{y} | y |
| x | \bar{x} 0 | 1 00 | 1 01 |
| | x 1 | 1 10 | 1 11 |

Simplifying Boolean Expressions

- Here, we've grouped all 4 (2^2) cells together
 - Just like we saw earlier, it doesn't matter what the values of x and y are- the function always results in 1

| | | y | |
|-----|-------------|----------------|----------------|
| | | \bar{y} | y |
| x | \bar{x} 0 | 1 00 | 1 01 |
| | x 1 | 1 10 | 1 11 |

Simplifying Boolean Expressions

- This is a three-variable K-Map
 - Notice that only one bit changes between each row and column

| | | z | |
|------------|---------------------|----------------|----------|
| | | \bar{z} 0 | z 1 |
| x y | $\bar{x}\bar{y}$ 00 | 0 000 | 0 001 |
| | $\bar{x}y$ 01 | 0 010 | 0 011 |
| | xy 11 | 0 110 | 0 111 |
| | $x\bar{y}$ 10 | 0 100 | 0 101 |

Simplifying Boolean Expressions

- Here's another SOP Expression from earlier:

$$\bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z + xy\bar{z} + xyz$$

| $x \ y \backslash z$ | | \bar{z} | z |
|----------------------|----|-----------|----------|
| | | 0 | 1 |
| $\bar{x} \bar{y}$ | 00 | 0 000 | 0 001 |
| $\bar{x} y$ | 01 | 1 010 | 0 011 |
| $x \bar{y}$ | 11 | 1 110 | 1 111 |
| $x y$ | 10 | 1 100 | 1 101 |

Simplifying Boolean Expressions

- First grouping (4 cells)
- Result is 1 when x is 1
 - y and z are irrelevant

| | | z | |
|------------|---------------------|----------------|----------|
| | | \bar{z} 0 | z 1 |
| x y | $\bar{x}\bar{y}$ 00 | 0 000 | 0 001 |
| | $\bar{x}y$ 01 | 1 010 | 0 011 |
| | xy 11 | 1 110 | 1 111 |
| | $x\bar{y}$ 10 | 1 100 | 1 101 |

Simplifying Boolean Expressions

- Second grouping (2 cells)
- Result is 1 when y is 1 and z is 0
 - x is irrelevant

| | | z | |
|------------|---------------------|----------------|----------|
| | | \bar{z} 0 | z 1 |
| x y | $\bar{x}\bar{y}$ 00 | 0 000 | 0 001 |
| | $\bar{x}y$ 01 | 1 010 | 0 011 |
| | xy 11 | 1 110 | 1 111 |
| | $x\bar{y}$ 10 | 1 100 | 1 101 |

Simplifying Boolean Expressions

- Result:


$$x + y\bar{z}$$

(Same as was derived with Boolean algebra)

| $\begin{matrix} & \mathbf{z} \\ \mathbf{x} \ \mathbf{y} & \end{matrix}$ | | \bar{z} | z |
|---|----|-----------|----------|
| | | 0 | 1 |
| $\bar{x}\bar{y}$ | 00 | 0 000 | 0 001 |
| $\bar{x}y$ | 01 | 1 010 | 0 011 |
| xy | 11 | 1 110 | 1 111 |
| $x\bar{y}$ | 10 | 1 100 | 1 101 |

Simplifying Boolean Expressions

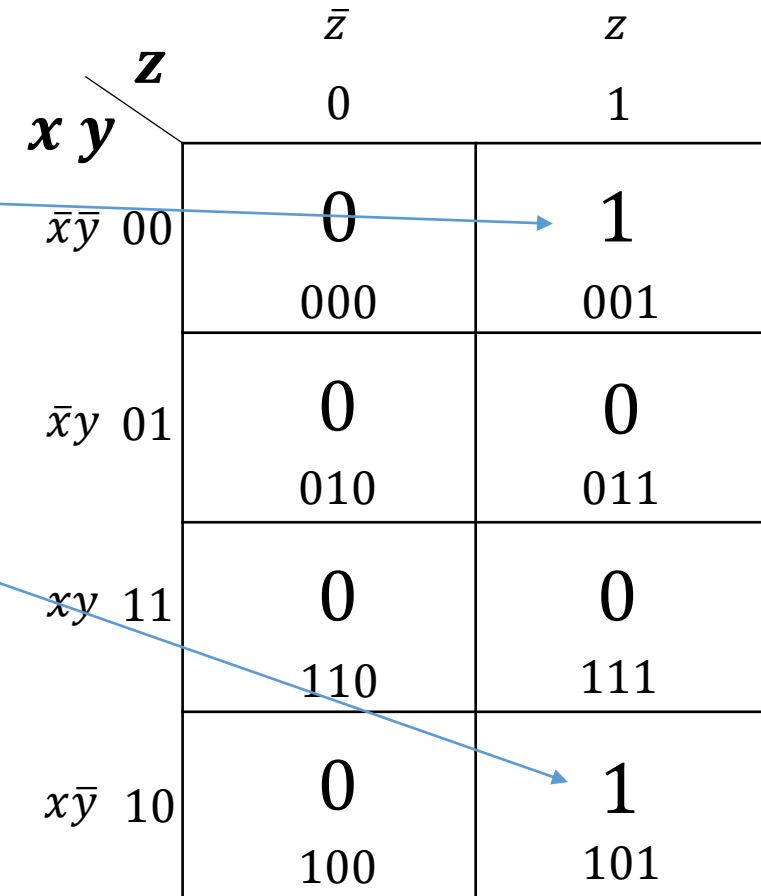- Another (new) SOP Expression:
 $x\bar{y}z + \bar{x}\bar{y}z$



| $\begin{matrix} z \\ x\ y \end{matrix}$ | | \bar{z} | z |
|---|----|-----------|----------|
| | | 0 | 1 |
| $\bar{x}\bar{y}$ | 00 | 0 000 | 1 001 |
| $\bar{x}y$ | 01 | 0 010 | 0 011 |
| xy | 11 | 0 110 | 0 111 |
| $x\bar{y}$ | 10 | 0 100 | 1 101 |

Simplifying Boolean Expressions

- Cell groups can wrap around the map
- Result is 1 when z is 1 and y is 0
 - x is irrelevant
- Result:


$$x\bar{y}z + \bar{x}\bar{y}z = \bar{y}z$$

| $\begin{matrix} & z \\ x & y \end{matrix}$ | | \bar{z} | z |
|--|----|-----------|----------|
| | | 0 | 1 |
| $\bar{x}\bar{y}$ | 00 | 0 000 | 1 001 |
| $\bar{x}y$ | 01 | 0 010 | 0 011 |
| xy | 11 | 0 110 | 0 111 |
| $x\bar{y}$ | 10 | 0 100 | 1 101 |

Simplifying Boolean Expressions

- Another (new) SOP Expression:
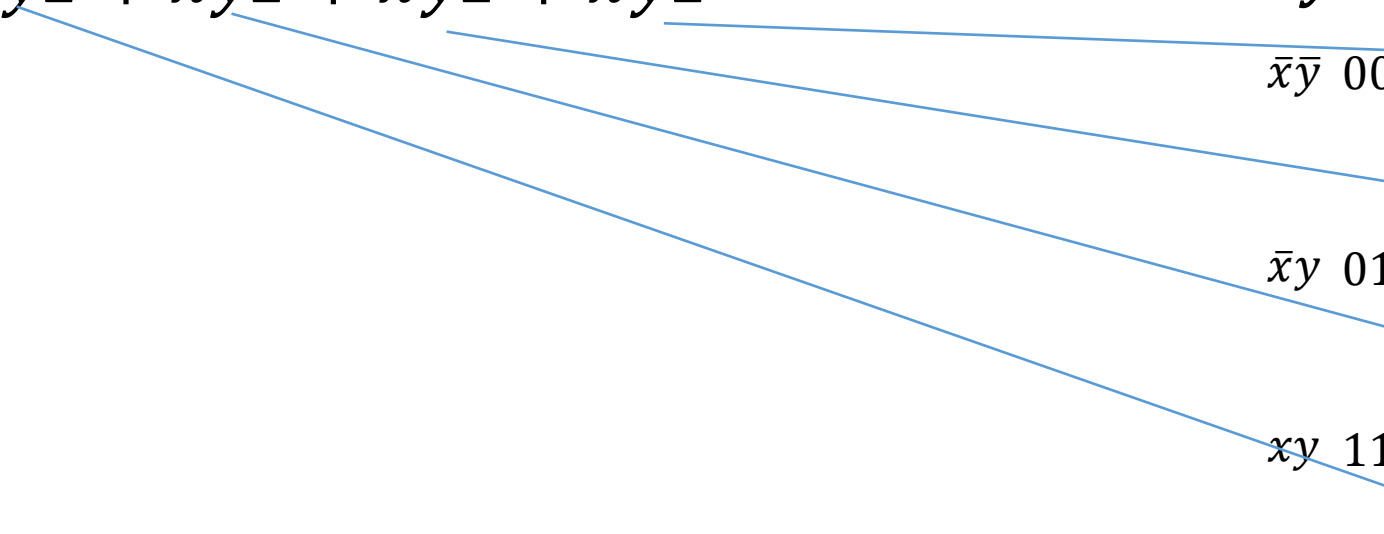
$$x\bar{y}z + xyz + \bar{x}yz + \bar{x}\bar{y}z$$



| | | z | |
|---------|---------------------|----------------|----------|
| | | \bar{z} 0 | z 1 |
| $x \ y$ | $\bar{x}\bar{y}$ 00 | 0 000 | 1 001 |
| | $\bar{x}y$ 01 | 0 010 | 1 011 |
| | xy 11 | 0 110 | 1 111 |
| | $x\bar{y}$ 10 | 0 100 | 1 101 |

Simplifying Boolean Expressions

- Cell grouping of 4
- Result is 1 when z is 1
 - x and y are irrelevant

- Result:

$$x\bar{y}z + xyz + \bar{x}yz + \bar{x}\bar{y}z = \mathbf{z}$$

| $\begin{matrix} & \mathbf{z} \\ \mathbf{x} \ \mathbf{y} & \swarrow \end{matrix}$ | | \bar{z} | z |
|--|----|-----------|----------|
| | | 0 | 1 |
| $\bar{x}\bar{y}$ | 00 | 0 000 | 1 001 |
| $\bar{x}y$ | 01 | 0 010 | 1 011 |
| xy | 11 | 0 110 | 1 111 |
| $x\bar{y}$ | 10 | 0 100 | 1 101 |

Simplifying Boolean Expressions

- Another (new) SOP Expression:

$$x\bar{y}\bar{z} + x\bar{y}z + \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z$$

| z $x\ y$ | | \bar{z} 0 | z 1 |
|------------------|----|----------------|----------|
| | | | |
| $\bar{x}\bar{y}$ | 00 | 1 000 | 1 001 |
| $\bar{x}y$ | 01 | 0 010 | 0 011 |
| xy | 11 | 0 110 | 0 111 |
| $x\bar{y}$ | 10 | 1 100 | 1 101 |

Simplifying Boolean Expressions

- Cell groups can wrap around the map

- Result is 1 when y is 0
 - x and z are irrelevant

- Result:

$$x\bar{y}\bar{z} + x\bar{y}z + \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z = \bar{y}$$

| | | z | |
|---------|---------------------|-----------|----------|
| | | \bar{z} | z |
| $x \ y$ | $\bar{x}\bar{y}$ 00 | 1 000 | 1 001 |
| | $\bar{x}y$ 01 | 0 010 | 0 011 |
| | xy 11 | 0 110 | 0 111 |
| | $x\bar{y}$ 10 | 1 100 | 1 101 |

Simplifying Boolean Expressions

- The usefulness of K-Maps for simplifying Boolean expressions should be apparent
- However, K-Maps will not explicitly show:
 - NAND Operations
 - NOR Operations
 - XOR Operations
 - XNOR Operations

Simplifying Boolean Expressions

- No groupings in this K-Map

- Result:

$$\bar{x}\bar{y} + xy$$

- Must recognize as XNOR

$$x \odot y$$

| | | y | |
|-----|-------------|-----------|---------|
| | | \bar{y} | y |
| x | \bar{x} 0 | 1 00 | 0 01 |
| | x 1 | 0 10 | 1 11 |

Simplifying Boolean Expressions

- Another ability of K-Maps are that it can ignore certain outputs.
- These outputs are called **don't cares**
- If there are certain inputs that we don't care about, we can still use those inputs in the simplification process

Simplifying Boolean Expressions

- Starting with a truth table...
- F represents the output of this function
- X represents outputs we don't care about
 - We don't what the output is for $x\bar{y}\bar{z}$ or xyz

| x | y | z | F |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | X |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | X |
| 1 | 1 | 1 | 1 |

Simplifying Boolean Expressions

- Building the K-Map

| x | y | z | F |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | X |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | X |
| 1 | 1 | 1 | 1 |

| | | z | |
|---------|----------------------|----------------|----------|
| | | \bar{z} 0 | z 1 |
| $x \ y$ | $\bar{x} \bar{y}$ 00 | 0 000 | 0 001 |
| | $\bar{x} y$ 01 | 1 010 | 1 011 |
| $x y$ | 11 | X 110 | 1 111 |
| | $x \bar{y}$ 10 | X 100 | 0 101 |

Simplifying Boolean Expressions

- Normally, we'd get the result:


$$\bar{x}y + yz$$

- But, we can use the don't cares as a 1 if it helps simplify further

| | | <i>z</i> | |
|---------------------------------------|----|-----------------|----------|
| | | \bar{z} 0 | z 1 |
| <i>x y</i> $\bar{x}\bar{y}$ | 00 | 0 000 | 0 001 |
| | 01 | 1 010 | 1 011 |
| xy | 11 | X 110 | 1 111 |
| | 10 | X 100 | 0 101 |

Simplifying Boolean Expressions

- Now, our result is: y

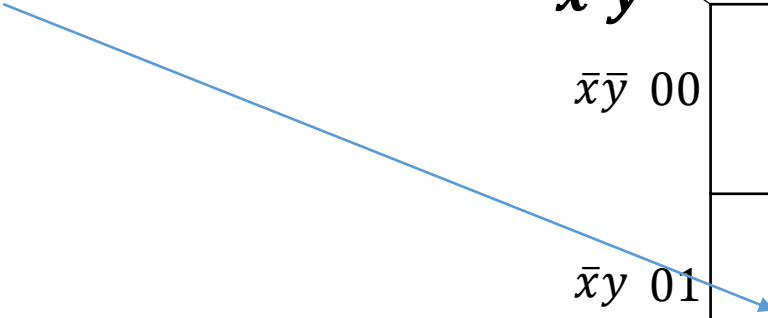

| | | z | |
|---------|---------------------|----------------|----------|
| | | \bar{z} 0 | z 1 |
| $x \ y$ | $\bar{x}\bar{y}$ 00 | 0 000 | 0 001 |
| | $\bar{x}y$ 01 | 1 010 | 1 011 |
| | xy 11 | X 110 | 1 111 |
| | $x\bar{y}$ 10 | X 100 | 0 101 |

Simplifying Boolean Expressions

- Checking with the truth table...
- Again, this function F doesn't care about the output for the inputs of $x\bar{y}\bar{z}$ or $xy\bar{z}$



| x | y | z | F | $\bar{x}y$ | yz | $\bar{x}y + yz$ |
|-----|-----|-----|-----|------------|------|-----------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | × | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | × | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 1 |

Logic Circuits

- The Boolean expressions we have been working with are the basis of constructing logic circuits.
- A **logic circuit** is a diagram of a Boolean expression.
- Logic circuits are built using **logic gates** that perform the different logical operations



Logic Circuits

- The AND Gate

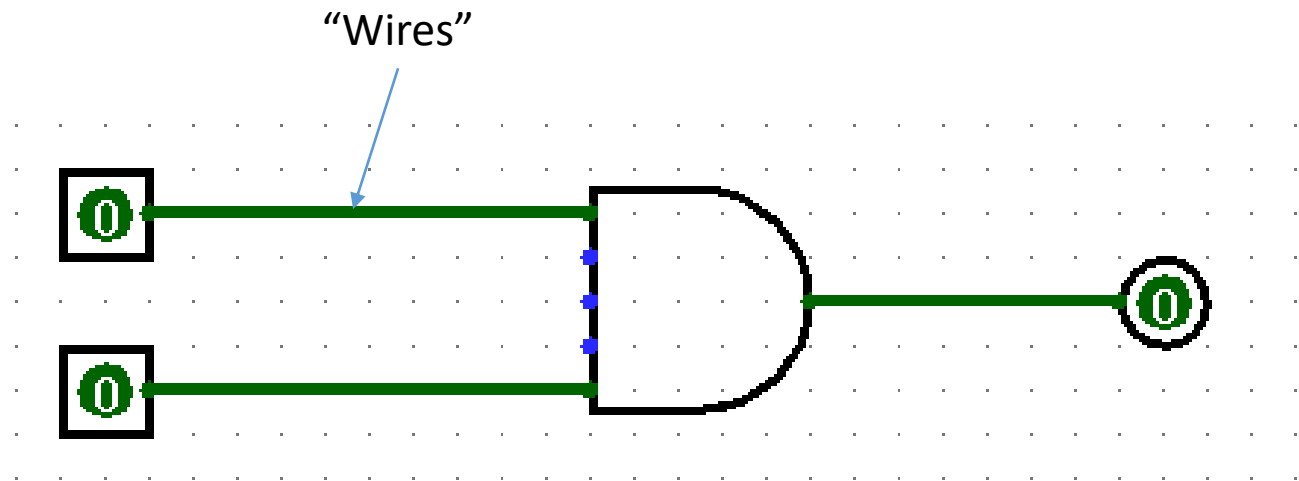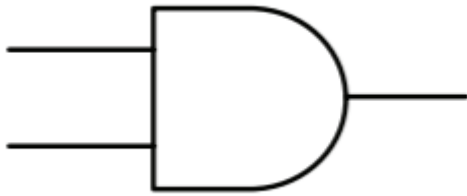



Logic Circuits

- The OR Gate

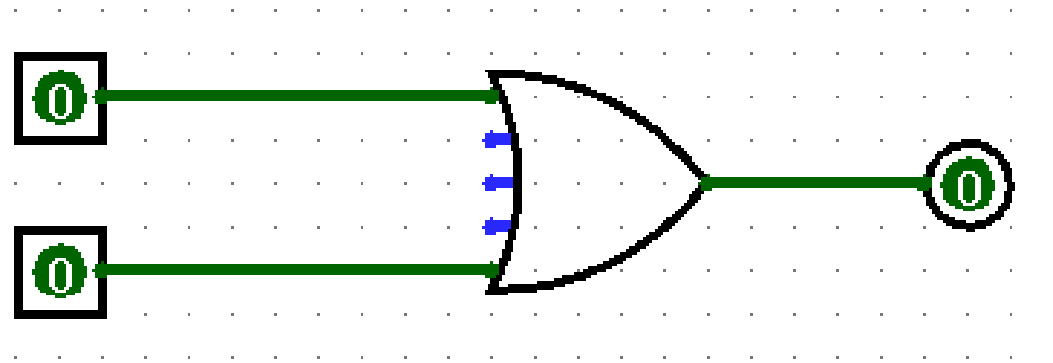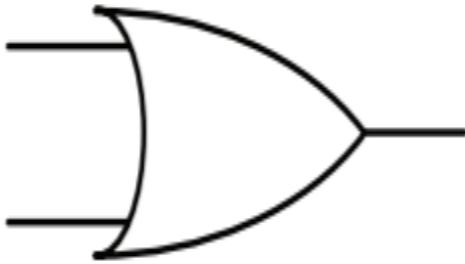



Logic Circuits

- The NOT Gate

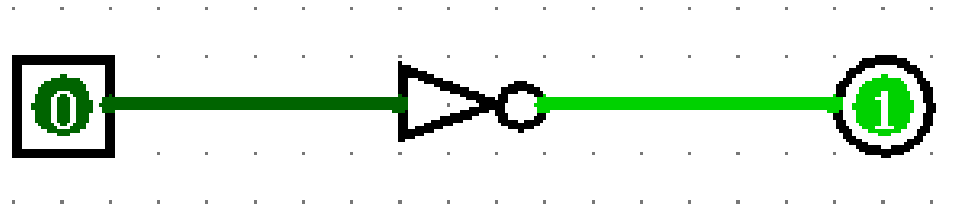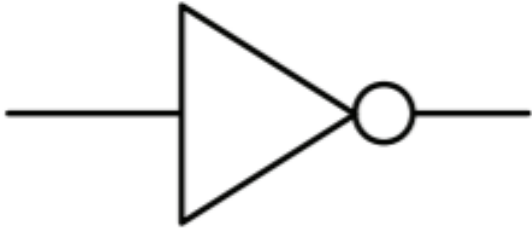



Logic Circuits

- The XOR Gate

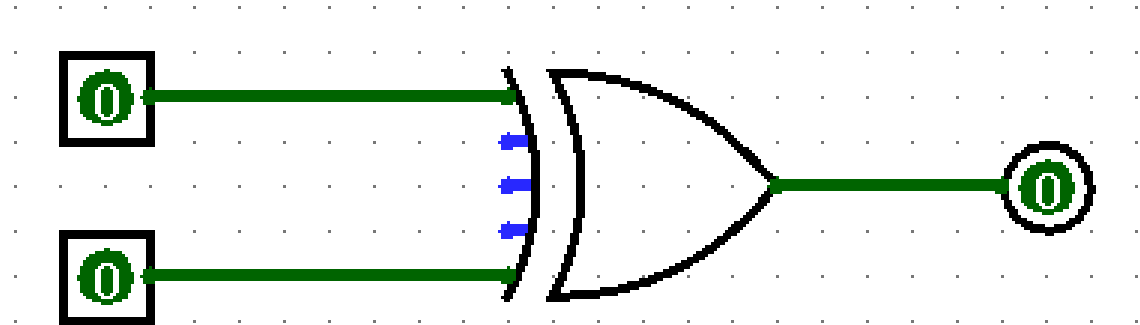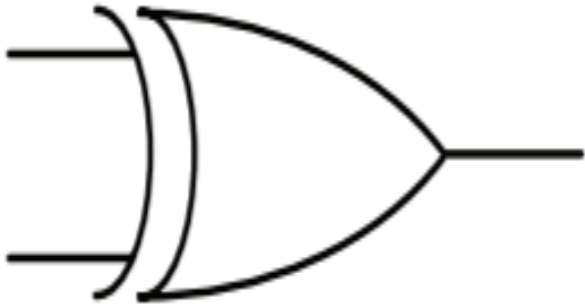



Logic Circuits

- The NOR Gate

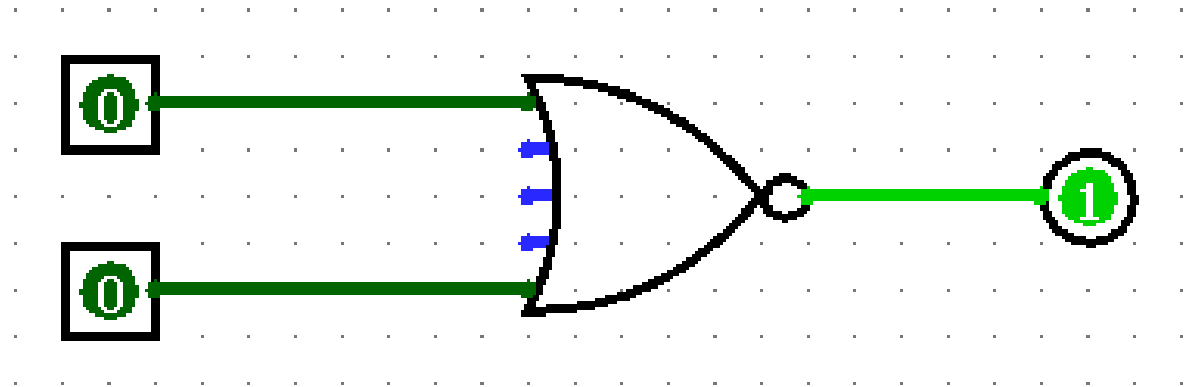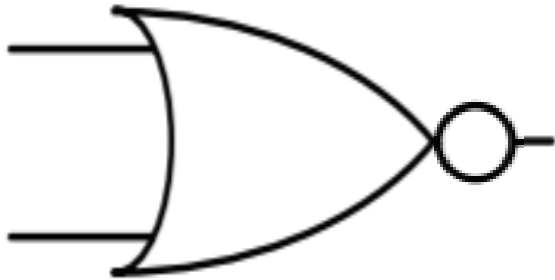



Logic Circuits

- The NAND Gate

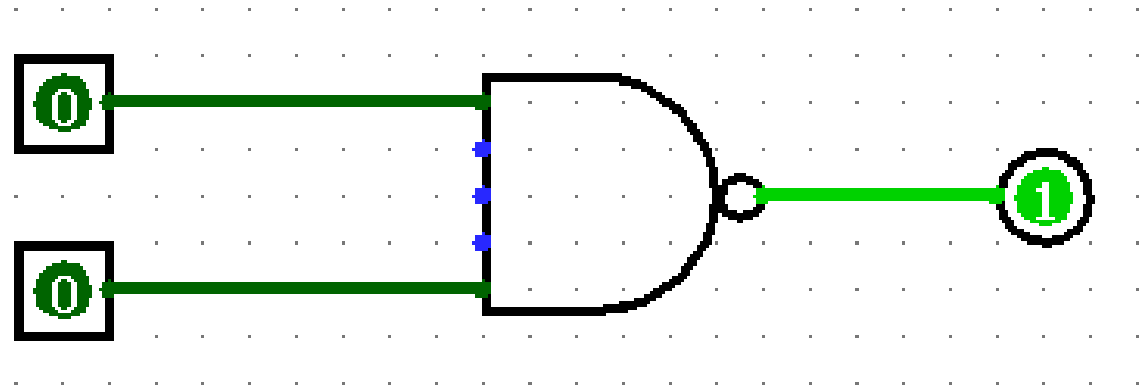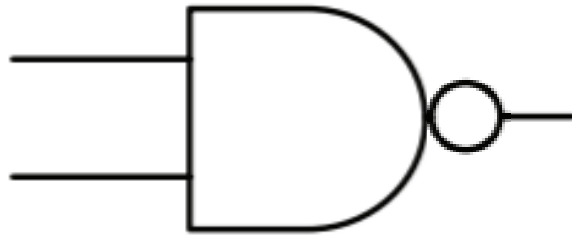


Logic Circuits

- The XNOR Gate

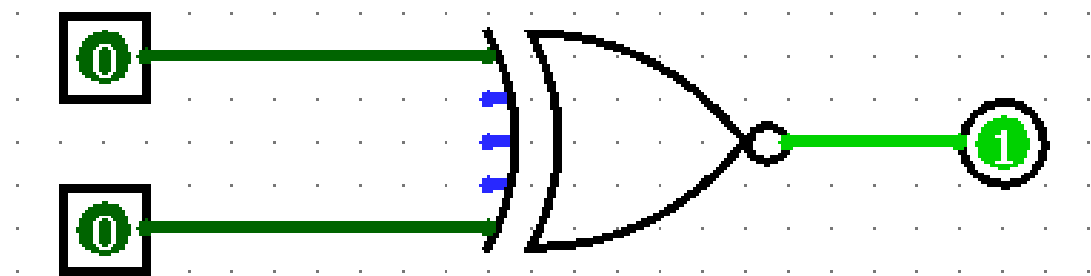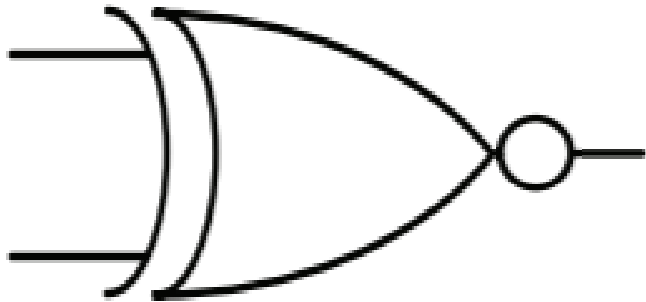


Logic Circuits

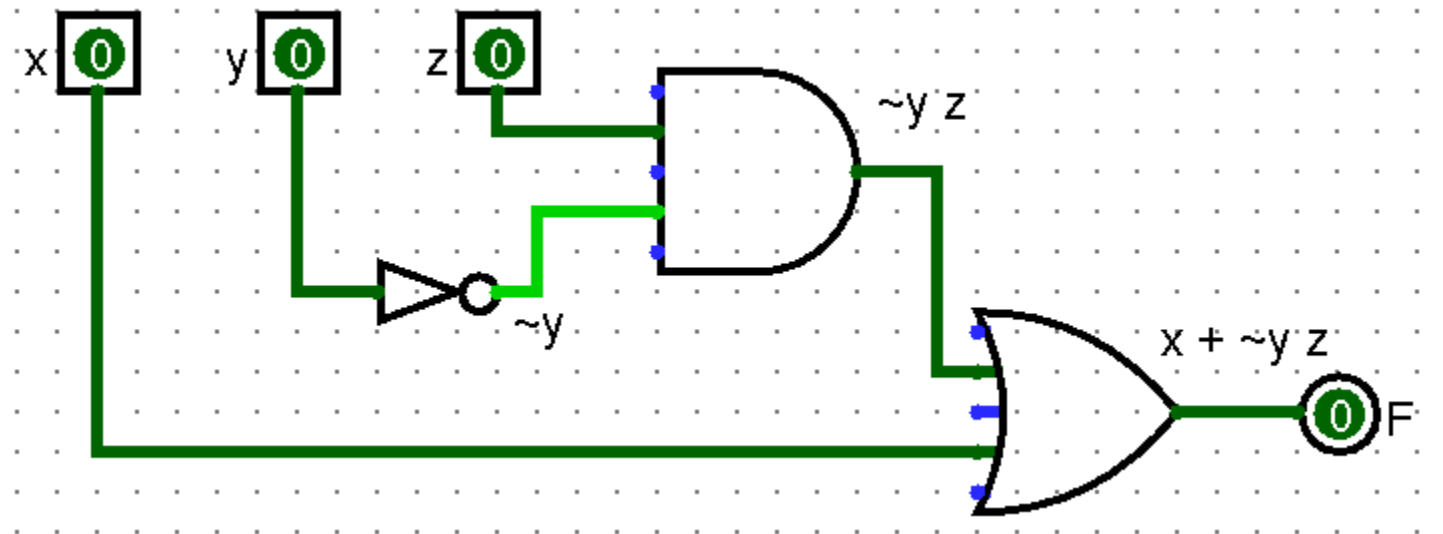- A logic circuit for the Boolean expression $x + \bar{y}z$
 - Be sure to follow order of operations




Logic Circuits

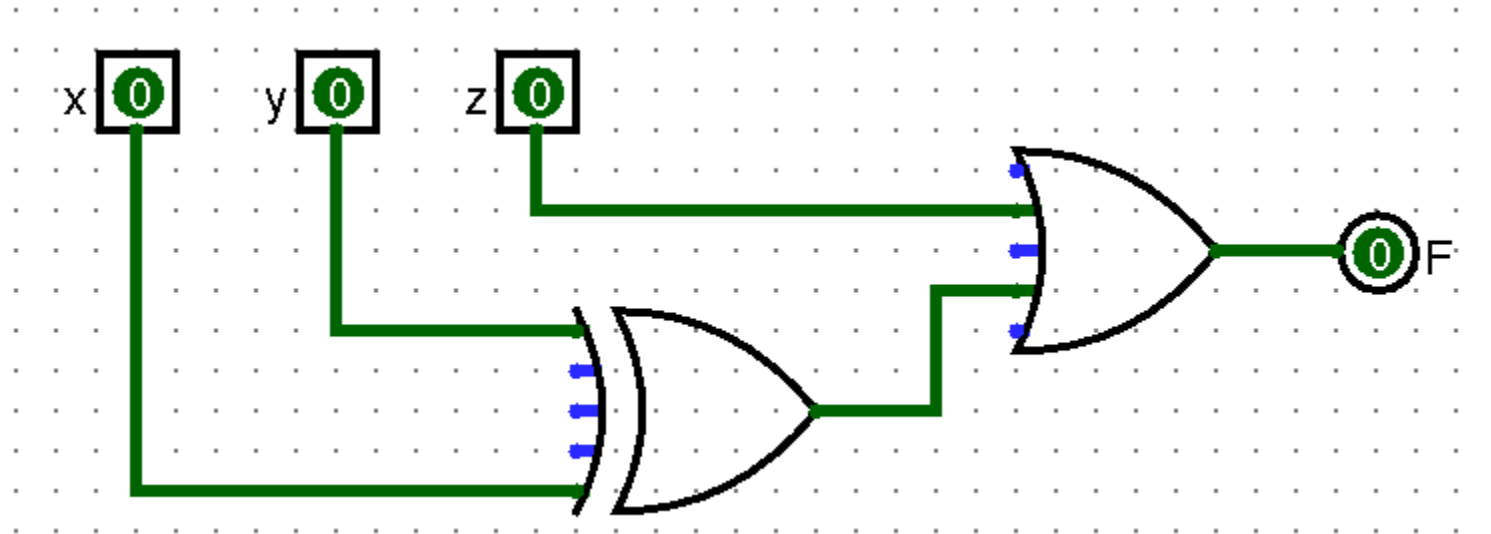- A logic circuit for the Boolean expression $x \oplus y + z$



Logic Circuits

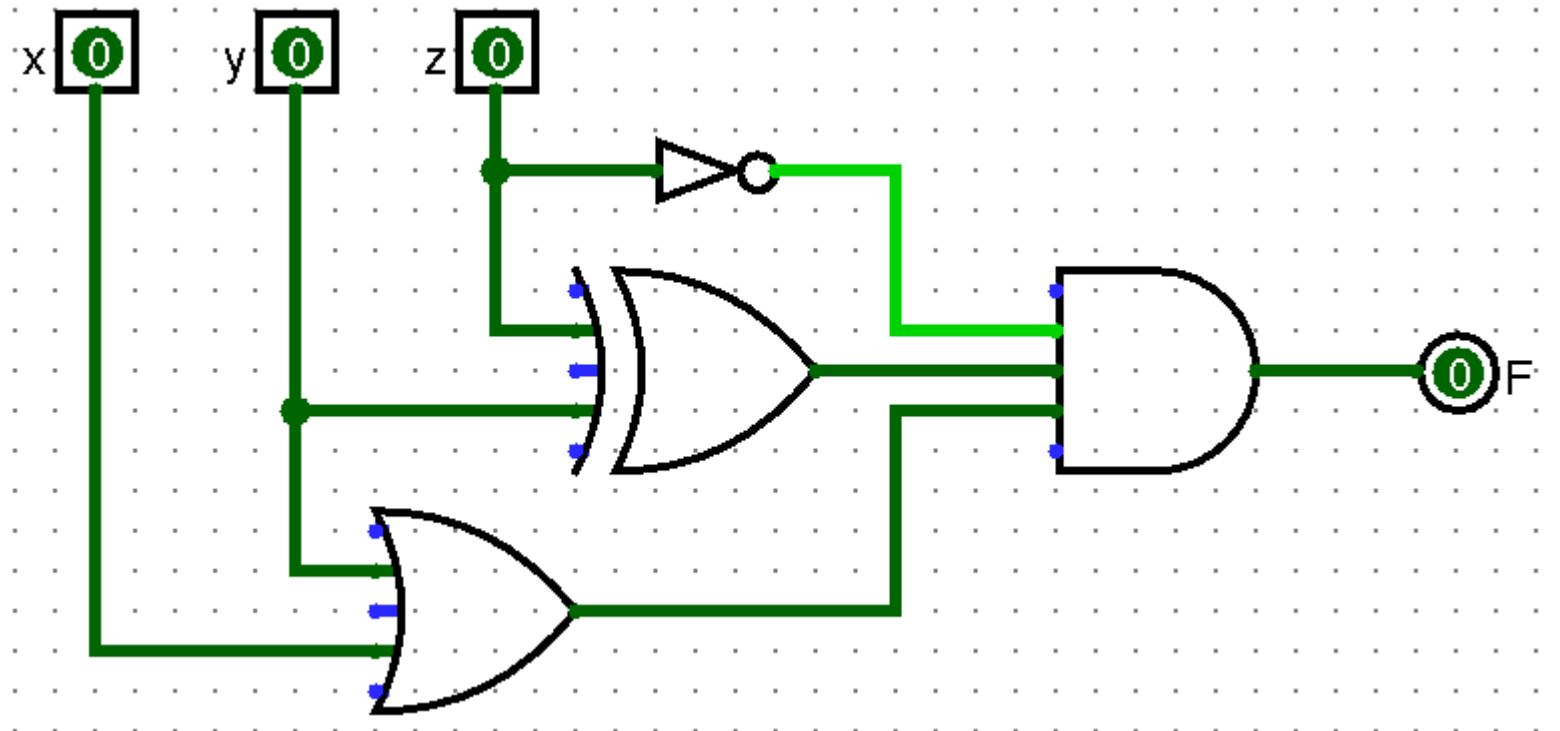- A logic circuit for the Boolean expression $(x + y)(y \oplus z)\bar{z}$




Buses

- A **bus** is several parallel wires going from one component to another.
- The bus's **width** is the number of parallel wires
- In a logic circuit, many parallel wires (like, say in a 32-bit bus) may make the diagram large and confusing


Buses

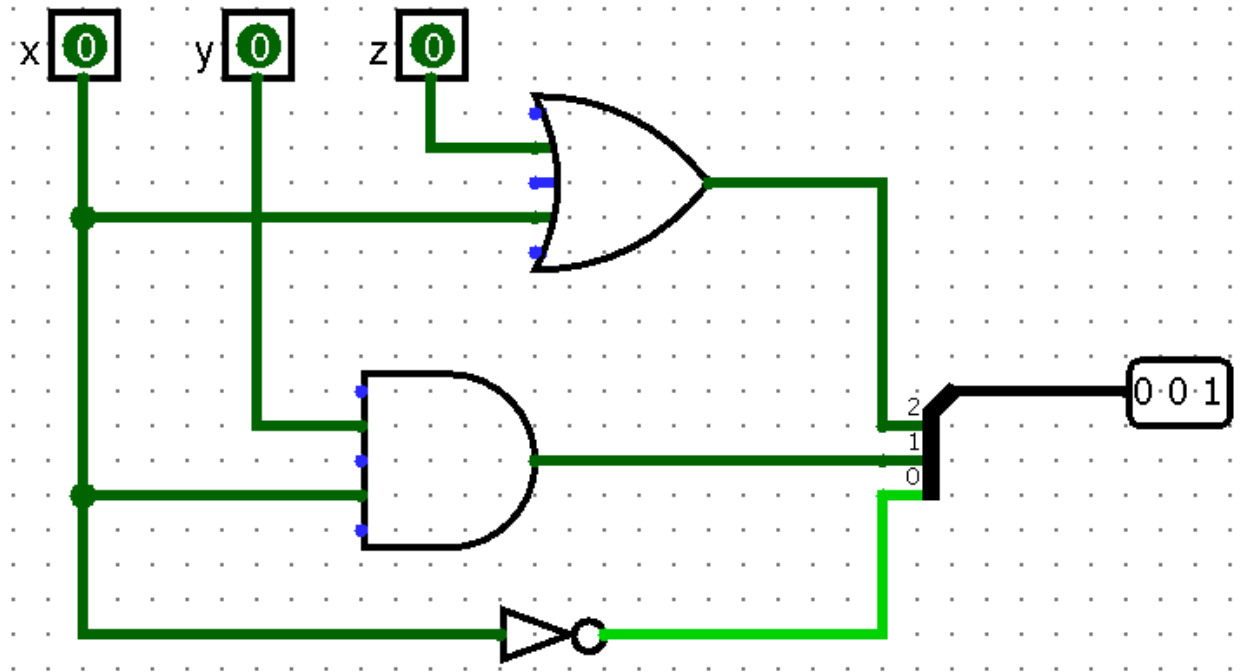- This circuit illustrates bundling three wires into one 3-bit bus



Buses

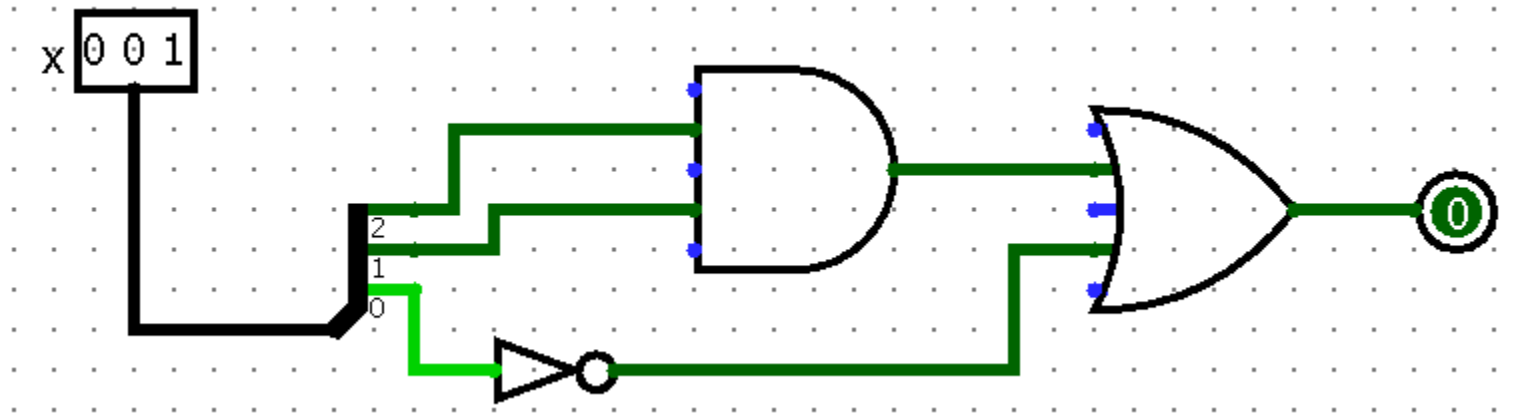- This circuit illustrates splitting the wires from a 3-bit bus




Sign Extend

- A sign extend is a combinational logic circuit that preserves the sign bit of a number on a bus when the bus's width is increased.
- For example, we'll say two 8-bit (two's complement) binary numbers 11001100 (negative) and 01010101 (positive) are sent on an 8-bit bus
- The bus's width is extended to 16-bits
 - A sign extend preserves the sign bit when this happens


Sign Extend

| Input Bus (8-bits) | Output Bus (16-bits) |
|--------------------|--------------------------|
| 11001100 | 11111111 11001100 |
| 01010101 | 00000000 01010101 |

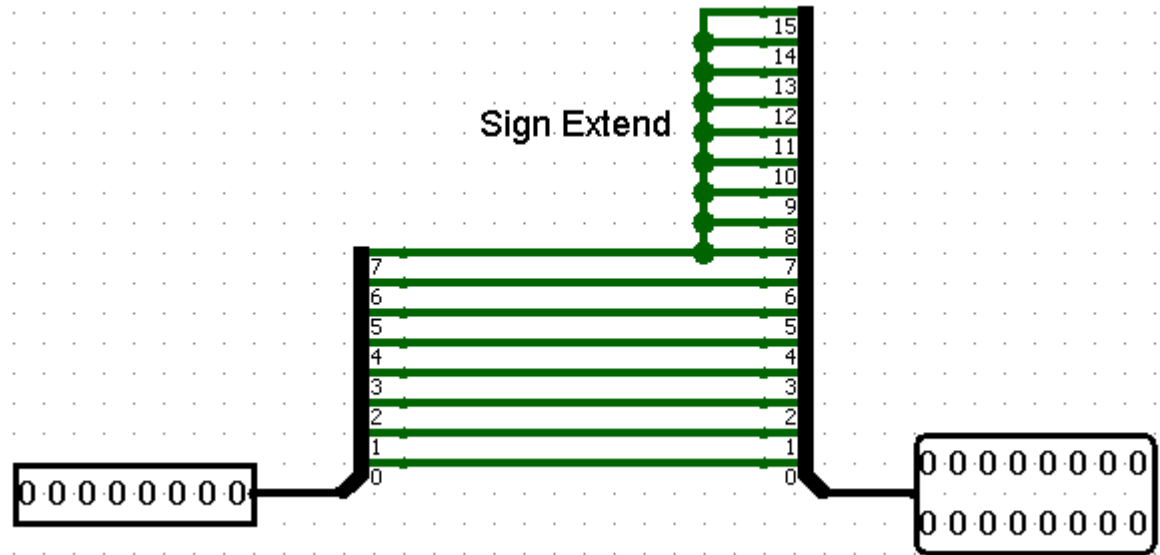


Sign Extend

| Input Bus (8-bits) | Output Bus (16-bits) |
|--------------------|--------------------------|
| 11001100 | 11111111 11001100 |
| 01010101 | 00000000 01010101 |

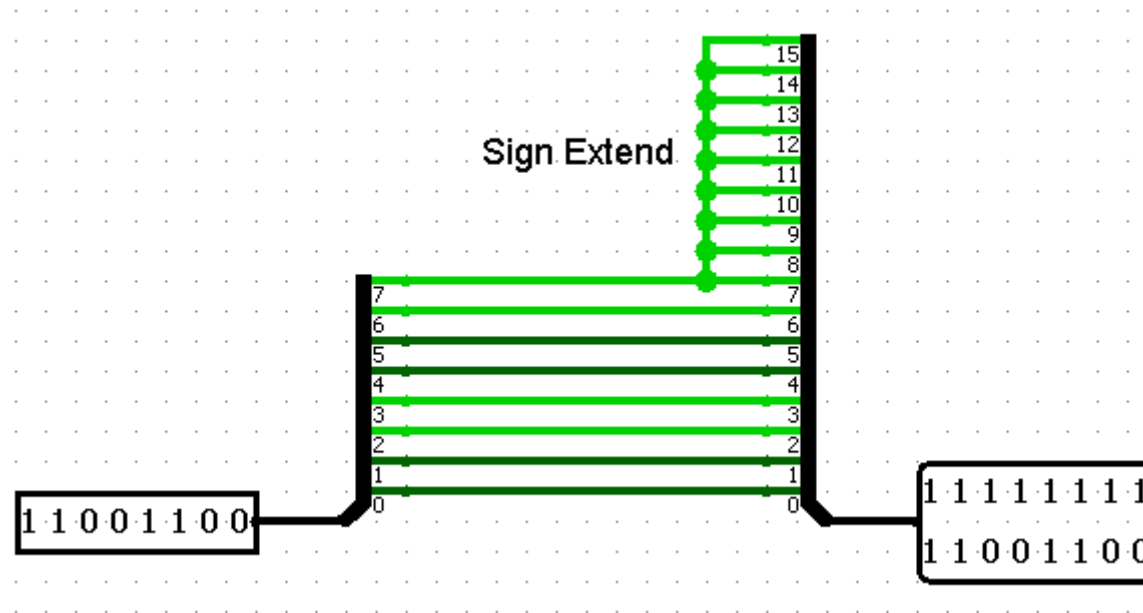

Sign Extend

| Input Bus (8-bits) | Output Bus (16-bits) |
|--------------------|--------------------------|
| 11001100 | 11111111 11001100 |
| 01010101 | 00000000 01010101 |

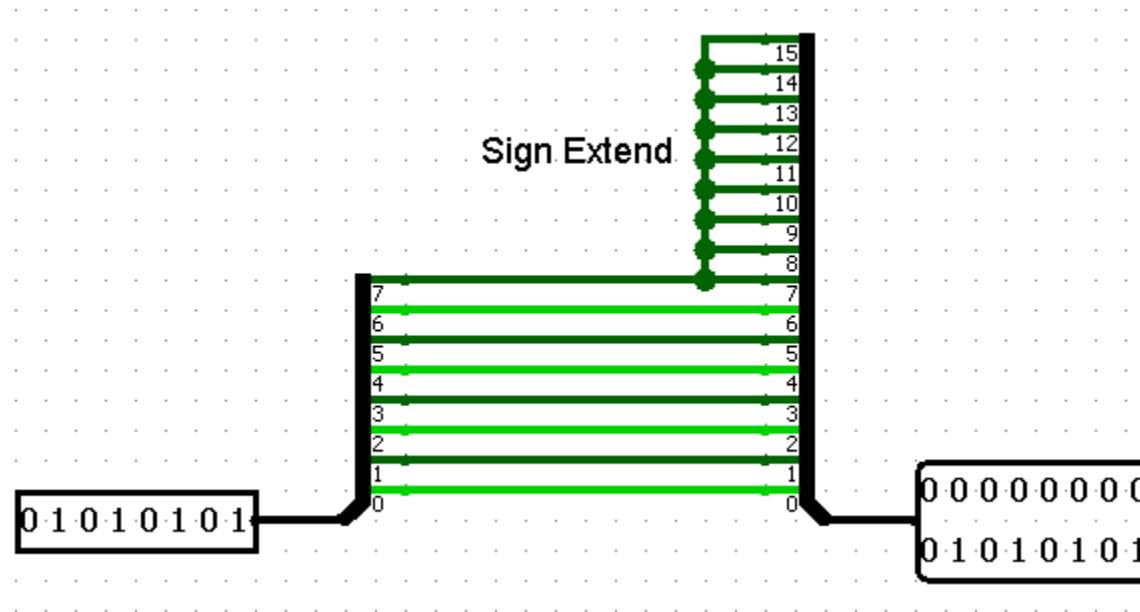


NAND-only/NOR-only Logic Circuits


- All the previously shown gates can be implemented using only NAND gates or implemented using only NOR gates
- NAND and NOR gates require fewer transistors than other gates, thus only using these gates will save room

Logic Circuits

- NAND-only AND gate:

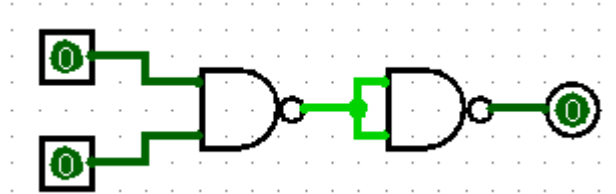


- NOR-only AND gate:

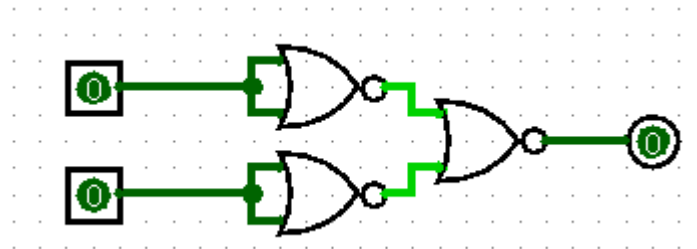


Logic Circuits

- NAND-only OR gate:

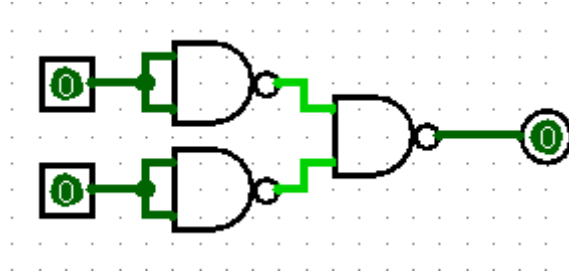

- NOR-only OR gate:

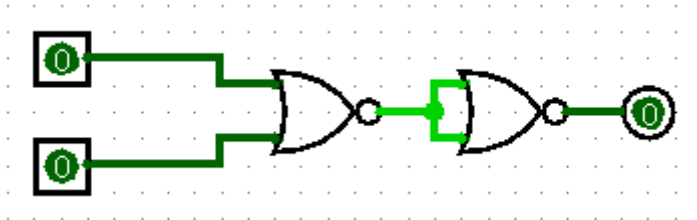

Logic Circuits

- NAND-only NOT gate:




- NOR-only NOT gate:




Logic Circuits

- NAND-only XOR gate:

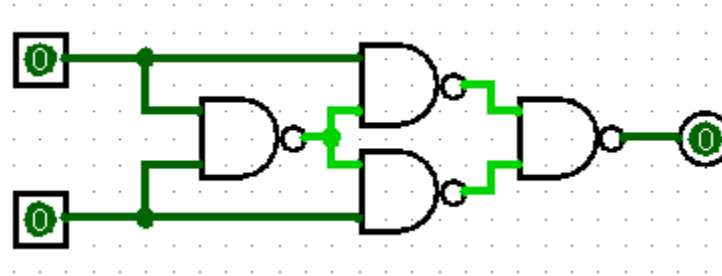


- NOR-only XOR gate:

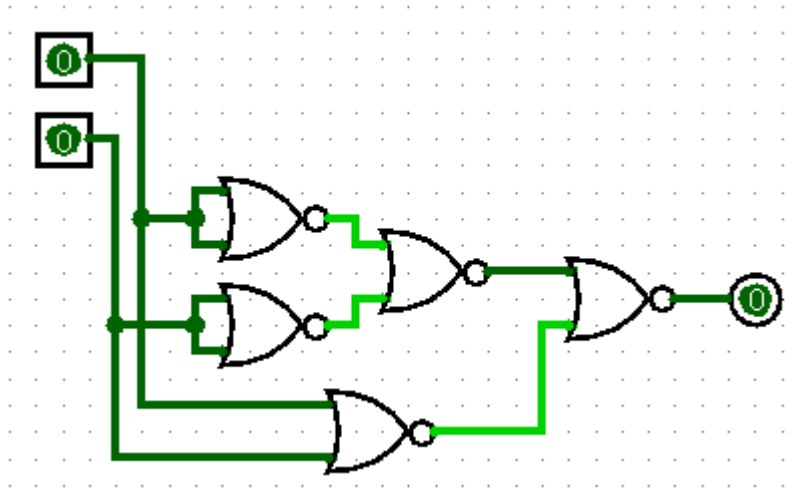


Logic Circuits

- NAND-only NOR gate:

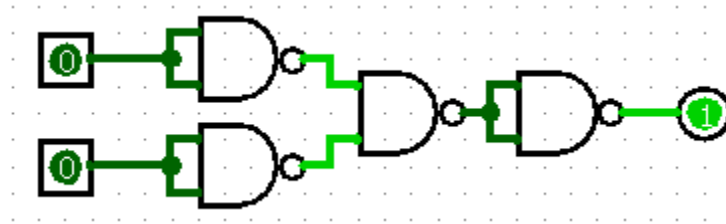


- NOR-only NAND gate:

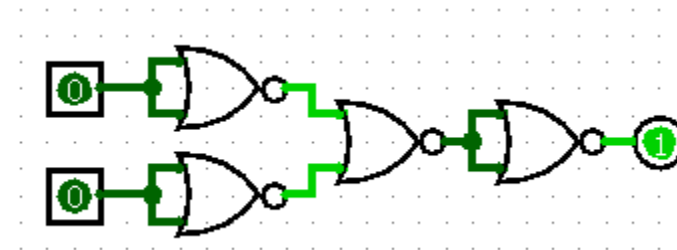

Logic Circuits

- NAND-only XNOR gate:

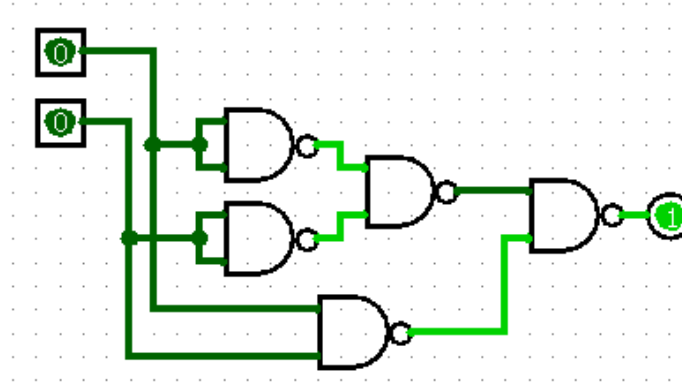

- NOR-only XNOR gate:

