

# Digital Logic II

Michael C. Hackett  
Assistant Professor, Computer Science

Community  
College  
*of* Philadelphia

# Lecture Topics

- Combinational Circuits
  - Sign Extend
  - Encoders
  - Decoders
  - Multiplexers
  - Demultiplexers

# Combinational Circuits


- We've seen the use of logic gates to implement a Boolean function
- With logic gates, we can build **combinational logic circuits** that can perform complex operations
  - They perform Boolean algebra on the circuit's input
- Combinational logic circuits are used in the construction of practical, digital computer circuits (including a computer's CPU)

# Sign Extend

- A sign extend is a combinational logic circuit that preserves the sign bit of a number on a bus when the bus's width is increased.
- For example, we'll say two 8-bit (two's complement) binary numbers 11001100 (negative) and 01010101 (positive) are sent on an 8-bit bus
- The bus's width is extended to 16-bits
  - A sign extend preserves the sign bit when this happens


# Sign Extend

Input Bus (8-bits)	Output Bus (16-bits)
11001100	<b>11111111</b> 11001100
01010101	<b>00000000</b> 01010101

 


# Sign Extend

Input Bus (8-bits)	Output Bus (16-bits)
<b>11001100</b>	<b>11111111 11001100</b>
01010101	00000000 01010101

 

# Sign Extend

Input Bus (8-bits)	Output Bus (16-bits)
11001100	11111111 11001100
<b>01010101</b>	<b>00000000 01010101</b>

 

# Encoders


- An encoder is a combinational logic circuit with  $2^n$  input pins and  $n$  output pins.
  - Only a single input pin is set to 1
- Below is the truth table for a 2x1 encoder
  - $I$  represents the input pins
  - $E$  represents the (encoded) output pins
- SOP Expression:  $I_1 \bar{I}_0$

$I_1$	$I_0$	$E_0$
0	1	0
1	0	1




# Encoders

- Logic circuit for a 2x1 encoder:

 

$I_1$	$I_0$	$E_0$
0	1	0
1	0	1

 

# Encoders


- Below is the truth table for a 4x2 encoder
  - $I$  represents the input pins
  - $E$  represents the (encoded) output pins

$I_3$	$I_2$	$I_1$	$I_0$	$E_1$	$E_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

- SOP Expression:  $E_1 = \bar{I}_3 I_2 \bar{I}_1 \bar{I}_0 + I_3 \bar{I}_2 \bar{I}_1 \bar{I}_0$
  - SOP Expression:  $E_0 = \bar{I}_3 \bar{I}_2 I_1 \bar{I}_0 + I_3 \bar{I}_2 \bar{I}_1 \bar{I}_0$
- ← Same term

# Encoders


- Logic circuit for a 4x2 encoder:

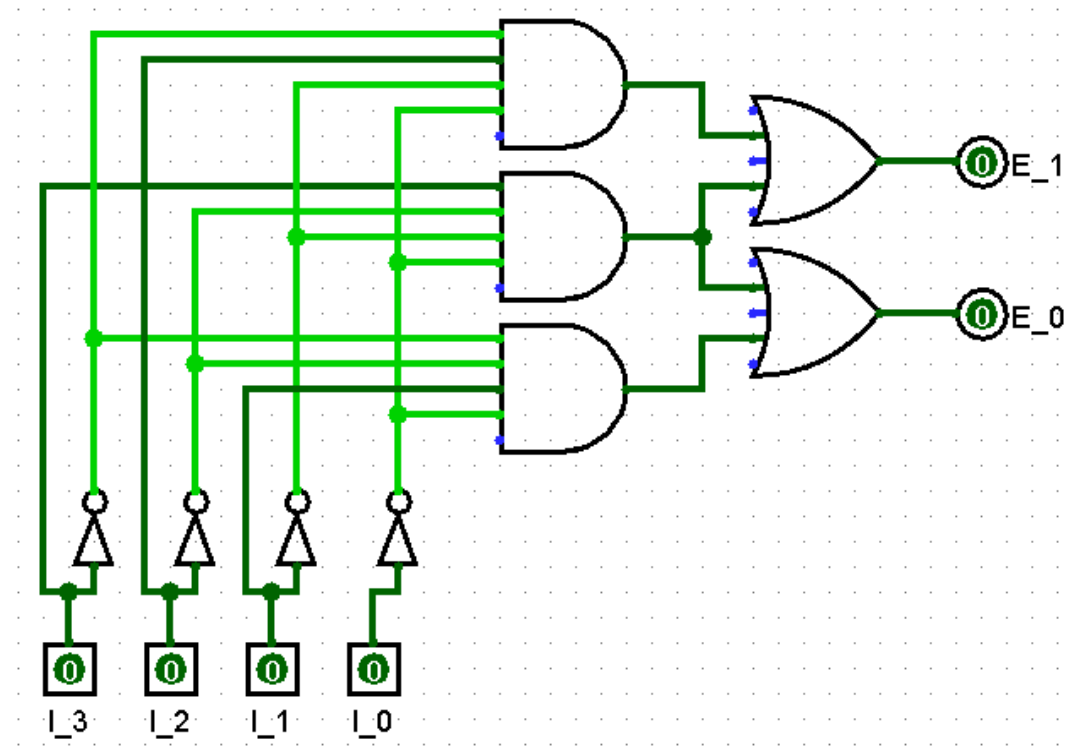

# Encoders

- Logic circuit for a 4x2 encoder:


$I_3$	$I_2$	$I_1$	$I_0$	$E_1$	$E_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

# Encoders

- Logic circuit for a 4x2 encoder:

$I_3$	$I_2$	$I_1$	$I_0$	$E_1$	$E_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

# Encoders

- Below is the truth table for an 8x3 encoder

$I_7$	$I_6$	$I_5$	$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$E_2$	$E_1$	$E_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

# Encoders


- SOP Expressions:

$$\begin{aligned} E_2 &= \bar{I}_7 \bar{I}_6 \bar{I}_5 I_4 \bar{I}_3 \bar{I}_2 \bar{I}_1 \bar{I}_0 + \boxed{\bar{I}_7 \bar{I}_6 I_5 \bar{I}_4 \bar{I}_3 \bar{I}_2 \bar{I}_1 \bar{I}_0} + \boxed{\bar{I}_7 I_6 \bar{I}_5 \bar{I}_4 \bar{I}_3 \bar{I}_2 \bar{I}_1 \bar{I}_0} + \boxed{I_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 \bar{I}_3 \bar{I}_2 \bar{I}_1 \bar{I}_0} \\ E_1 &= \bar{I}_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 \bar{I}_3 I_2 \bar{I}_1 \bar{I}_0 + \boxed{\bar{I}_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 I_3 \bar{I}_2 \bar{I}_1 \bar{I}_0} + \boxed{\bar{I}_7 I_6 \bar{I}_5 \bar{I}_4 \bar{I}_3 \bar{I}_2 \bar{I}_1 \bar{I}_0} + \boxed{I_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 \bar{I}_3 \bar{I}_2 \bar{I}_1 \bar{I}_0} \\ E_0 &= \bar{I}_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 \bar{I}_3 \bar{I}_2 I_1 \bar{I}_0 + \boxed{\bar{I}_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 I_3 \bar{I}_2 \bar{I}_1 \bar{I}_0} + \boxed{\bar{I}_7 \bar{I}_6 I_5 \bar{I}_4 \bar{I}_3 \bar{I}_2 \bar{I}_1 \bar{I}_0} + \boxed{I_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 \bar{I}_3 \bar{I}_2 \bar{I}_1 \bar{I}_0} \end{aligned}$$

- (Boxed terms indicate duplicates)

# Encoders

- Logic circuit for an 8x3 encoder:

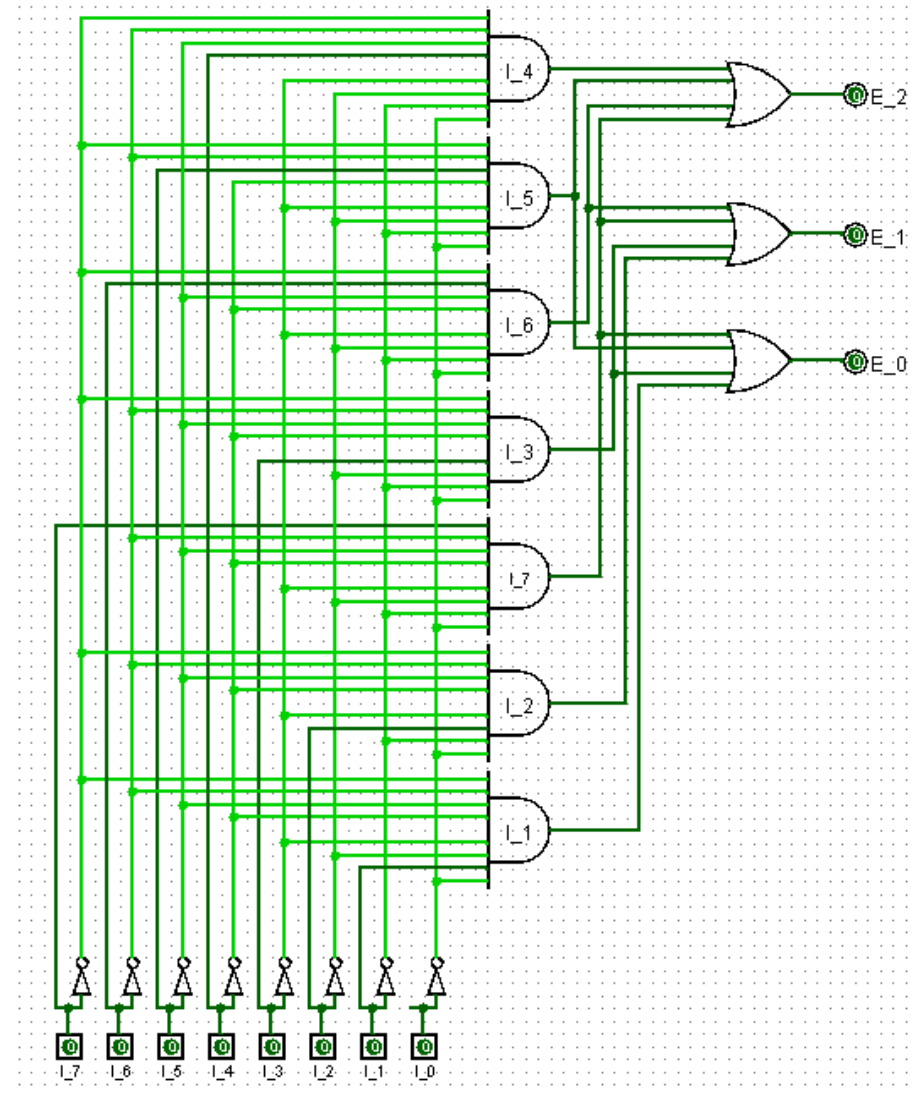




# Encoders

- Logic circuit for an 8x3 encoder:


$I_7$	$I_6$	$I_5$	$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$E_2$	$E_1$	$E_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

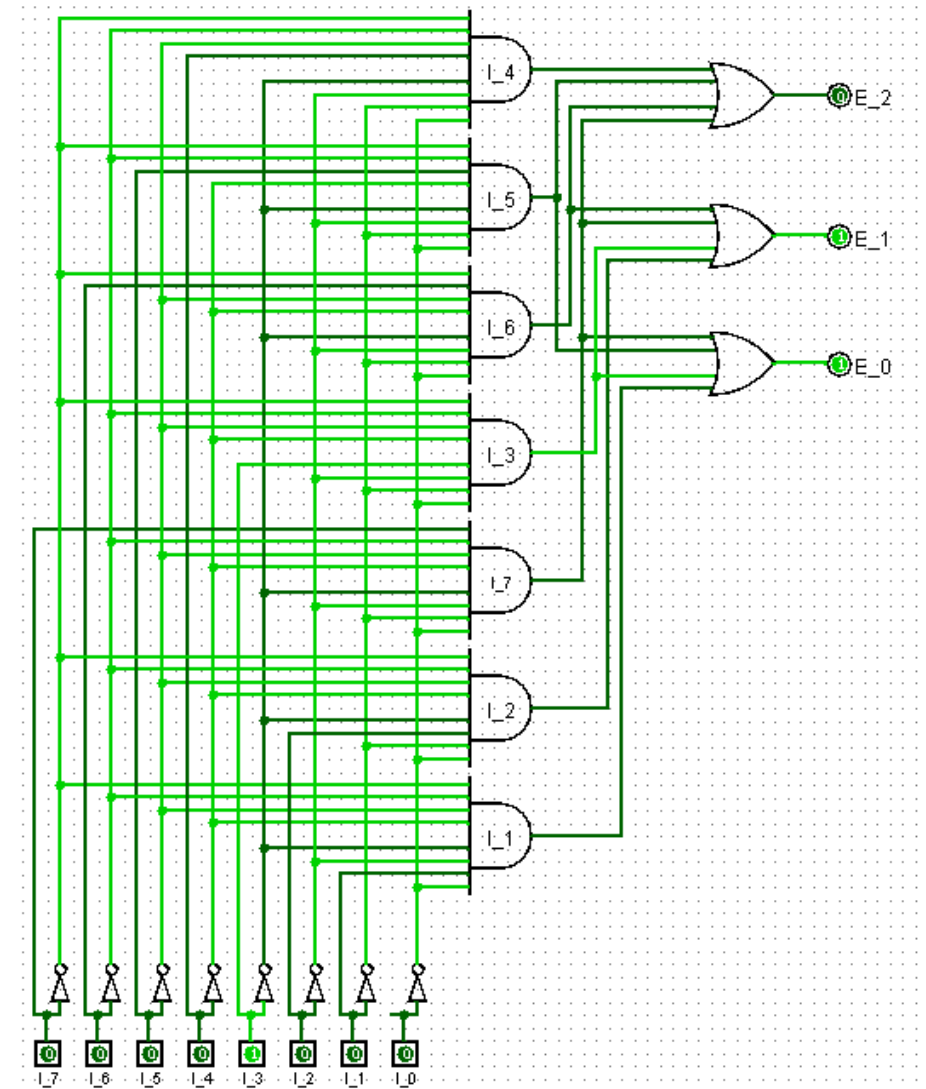

# Encoders

- Logic circuit for an 8x3 encoder:


$I_7$	$I_6$	$I_5$	$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$E_2$	$E_1$	$E_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

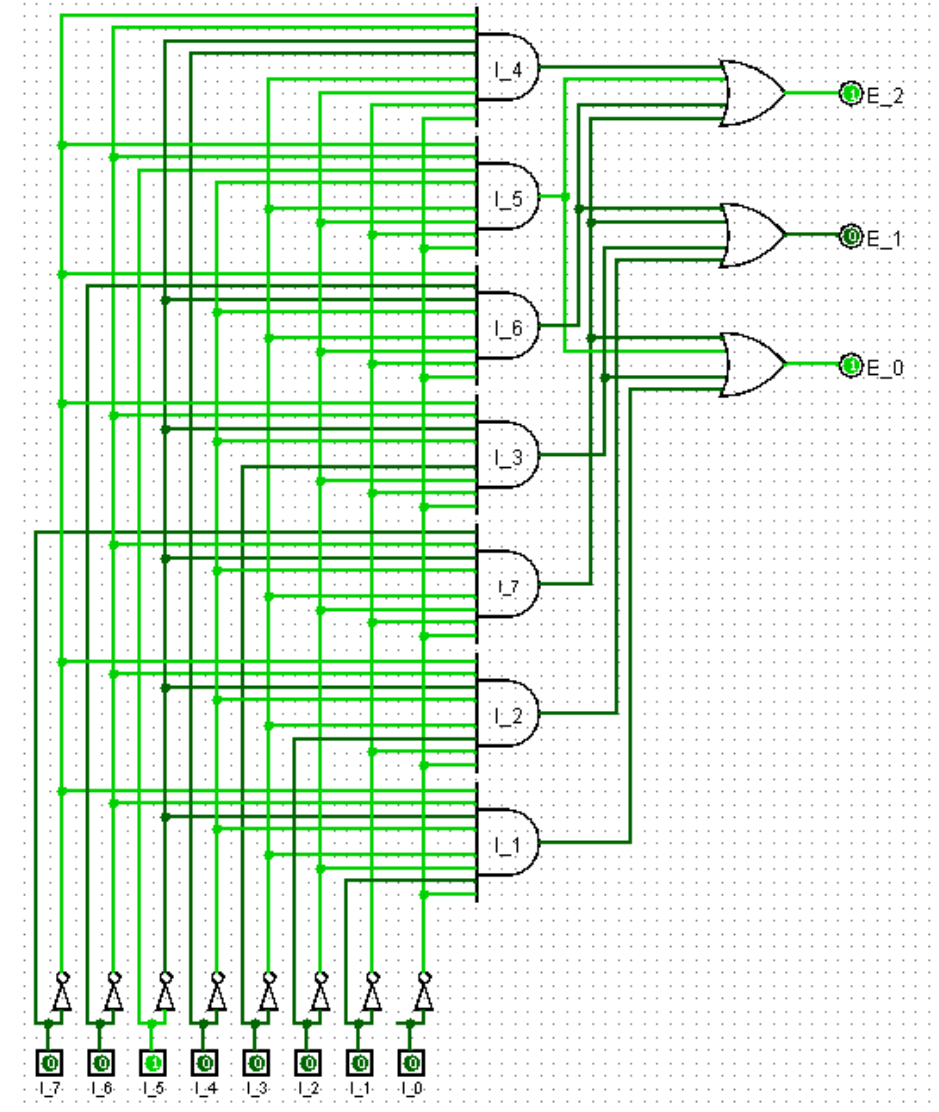

# Encoders

- Logic circuit for an 8x3 encoder:

$I_7$	$I_6$	$I_5$	$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$E_2$	$E_1$	$E_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

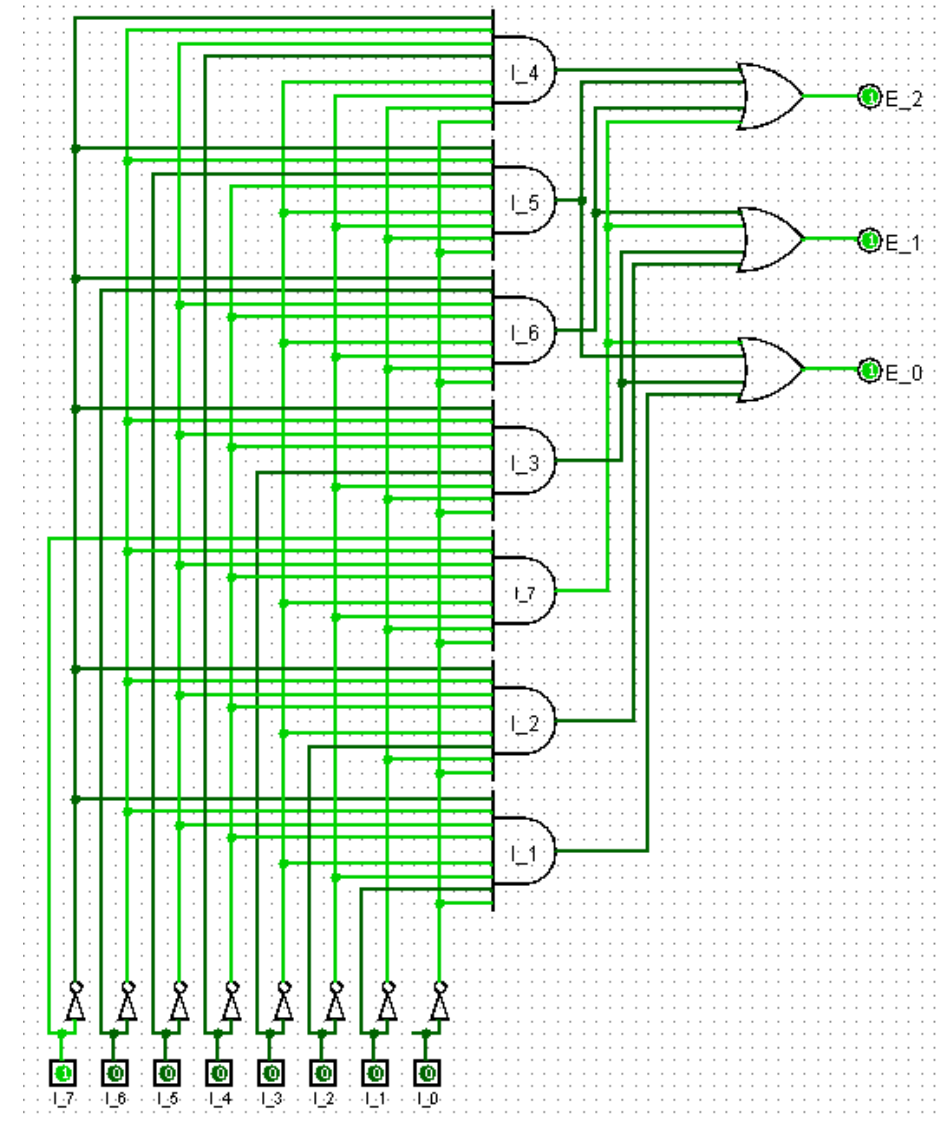

# Decoders

- A decoder is a combinational logic circuit with  $n$  input pins and  $2^n$  output pins.
  - For each output, only a single bit is set to 1

- Below is the truth table for a 1x2 decoder

- $I$  represents the input pins
- $D$  represents the (decoded) output pins

$I_0$	$D_1$	$D_0$
0	1	0
1	0	1


- SOP Expressions:

$$D_0 = I_0$$


$$D_1 = \overline{I_0}$$

# Decoders

- Logic circuit for a 1x2 decoder:

 

$I_0$	$D_1$	$D_0$
0	1	0
1	0	1

 

# Decoders

- Below is the truth table for a 2x4 decoder
  - ***I*** represents the input pins
  - ***D*** represents the (decoded) output pins

- SOP Expressions:

$$D_0 = \overline{I_1} \overline{I_0}$$

$$D_1 = \overline{I_1} I_0$$


$$D_2 = I_1 \overline{I_0}$$

$$D_3 = I_1 I_0$$

$I_1$	$I_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

# Decoders


- Logic circuit for a 2x4 decoder:

 

# Decoders

- Logic circuit for a 2x4 decoder:

$I_1$	$I_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 




# Decoders

- Logic circuit for a 2x4 decoder:

$I_1$	$I_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

# Decoders

- Below is the truth table for a 3x8 decoder

$I_2$	$I_1$	$I_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

# Decoders

- SOP Expressions:

$$D_0 = \bar{I}_2 \bar{I}_1 \bar{I}_0$$

$$D_1 = \bar{I}_2 \bar{I}_1 I_0$$

$$D_2 = \bar{I}_2 I_1 \bar{I}_0$$

$$D_3 = \bar{I}_2 I_1 I_0$$

$$D_4 = I_2 \bar{I}_1 \bar{I}_0$$


$$D_5 = I_2 \bar{I}_1 I_0$$

$$D_6 = I_2 I_1 \bar{I}_0$$

$$D_7 = I_2 I_1 I_0$$

# Decoders


- Logic circuit for a 3x8 decoder:

 

# Decoders

- Logic circuit for a 3x8 decoder:


$I_2$	$I_1$	$I_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

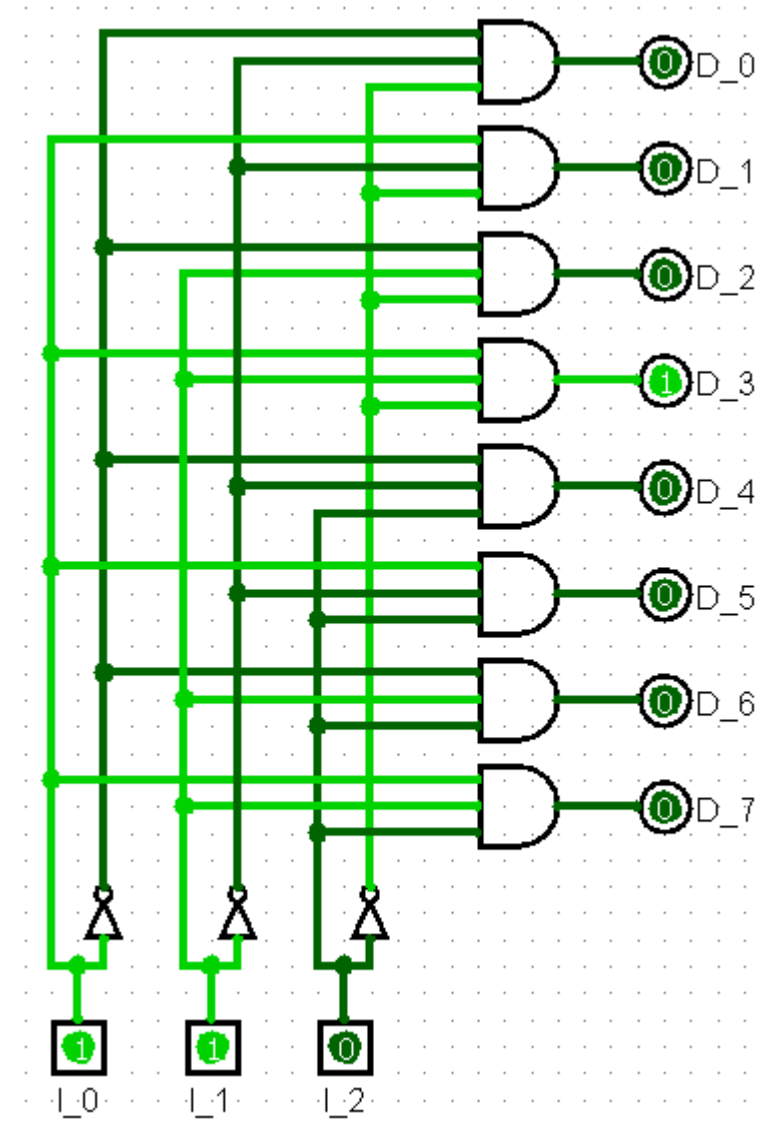

# Decoders

- Logic circuit for a 3x8 decoder:

$I_2$	$I_1$	$I_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

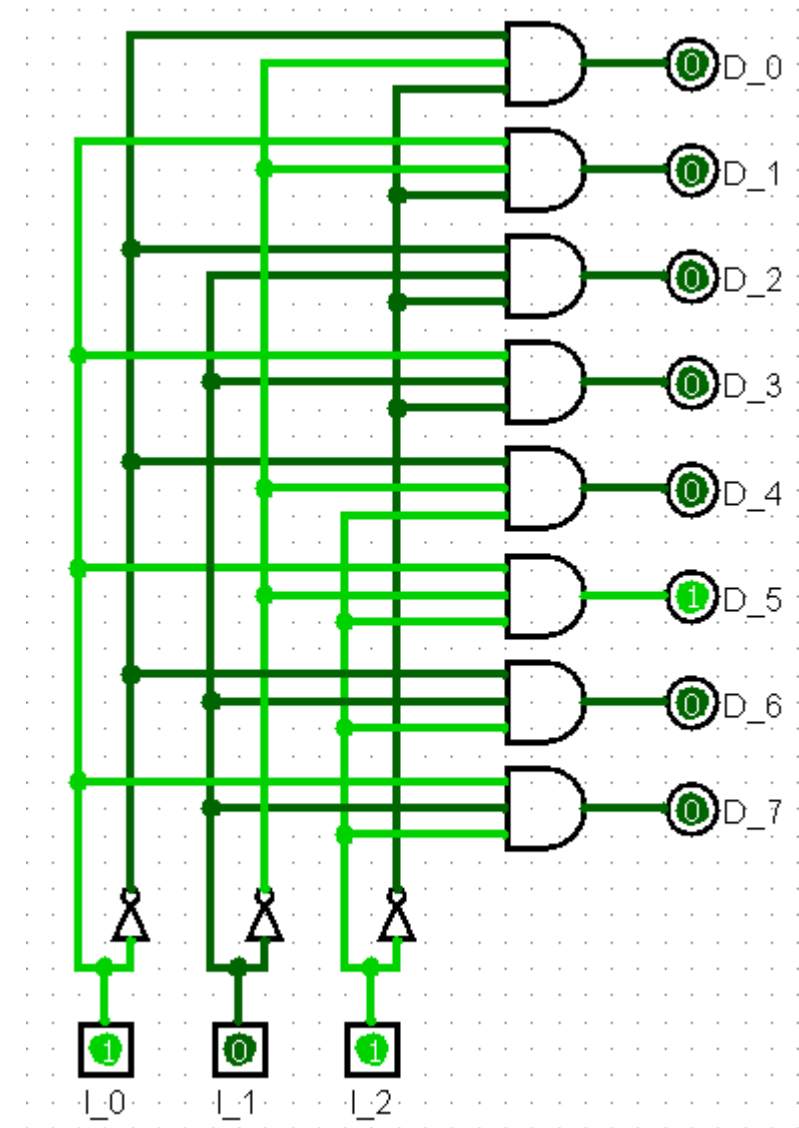

# Multiplexers

- A multiplexer (*MUX*) is a combinational logic circuit used to select one of multiple input lines
- A multiplexer has  $2^n$  input pins,  $n$  select pins, and 1 output pin.
  - The output is one of the input pins


- The truth table for a 4x1 multiplexer:
  - *I* represents the input pins ( $4 = 2^2$ )
  - *S* represents the select pins (**2**)
  - *M* represents the output pin

<i>S</i> <sub>1</sub>	<i>S</i> <sub>0</sub>	<i>M</i>
0	0	<i>I</i> <sub>0</sub>
0	1	<i>I</i> <sub>1</sub>
1	0	<i>I</i> <sub>2</sub>
1	1	<i>I</i> <sub>3</sub>

$$\text{SOP Expression: } M = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

# Multiplexers


- Logic circuit for a 4x1 multiplexer:

 



# Multiplexers

- Abstracted 4x1 multiplexer:

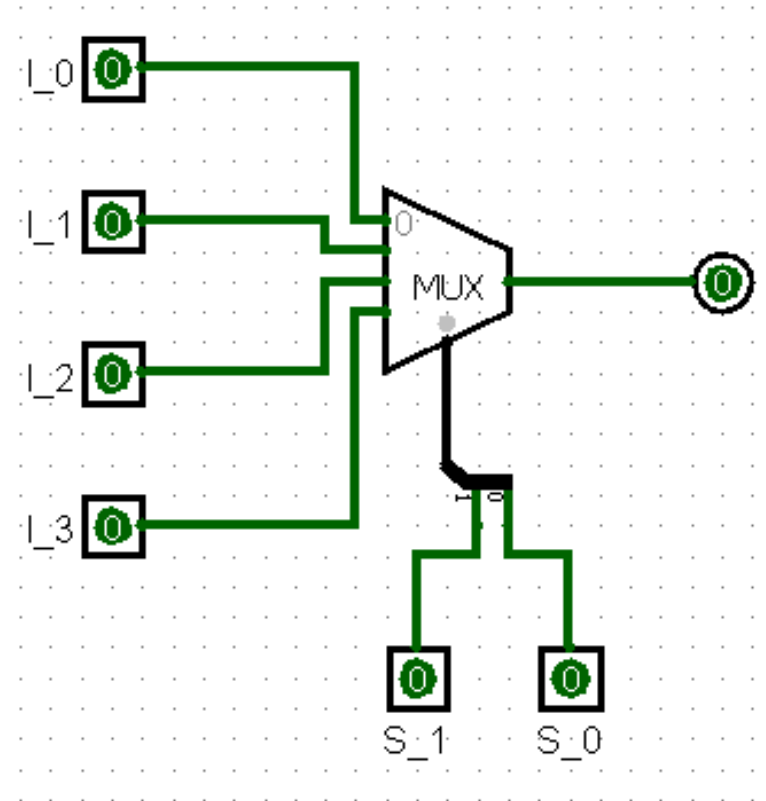

# Multiplexers

- The truth table for an 8x1 multiplexer:
  - ***I*** represents the input pins ( $8 = 2^3$ )
  - ***S*** represents the select pins (**3**)
  - ***M*** represents the output pin


$S_2$	$S_1$	$S_0$	$M$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

SOP Expression:

$$M = \bar{S}_2 \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_2 \bar{S}_1 S_0 I_1 + \bar{S}_2 S_1 \bar{S}_0 I_2 + \bar{S}_2 S_1 S_0 I_3 + S_2 \bar{S}_1 \bar{S}_0 I_4 + S_2 \bar{S}_1 S_0 I_5 + S_2 S_1 \bar{S}_0 I_6 + S_2 S_1 S_0 I_7$$


# Multiplexers

- Logic circuit for an 8x1 multiplexer:

 

# Multiplexers

- Abstracted 8x1 multiplexer:

 


# Multiplexers

- Buses can be inputs and outputs of a multiplexer.
  - A multiplexer with  $s$  select lines and  $n$ -bit buses is a  $2^s \times n$  multiplexer
- For example, a multiplexer with 2 select lines (implying 4 inputs) where each input is a 4-bit bus
  - $2^s \times n = 2^2 \times 4 = 4 \times 4$  multiplexer

# Multiplexers

- 4x4 Multiplexer:


$S_1$	$S_0$	$M$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

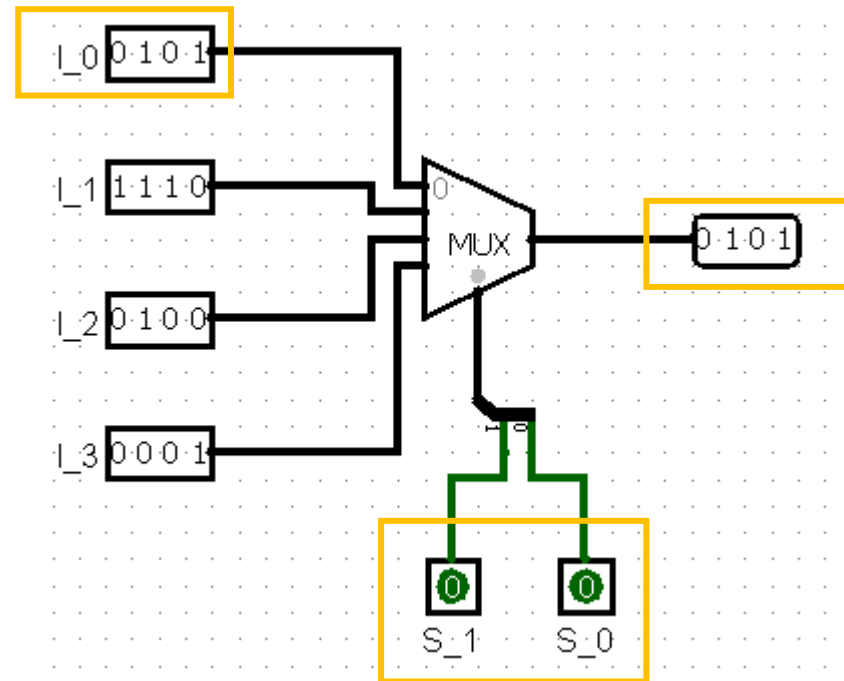

# Multiplexers

- 4x4 Multiplexer:


$S_1$	$S_0$	$M$
0	0	$I_0$
<b>0</b>	<b>1</b>	<b><math>I_1</math></b>
1	0	$I_2$
1	1	$I_3$

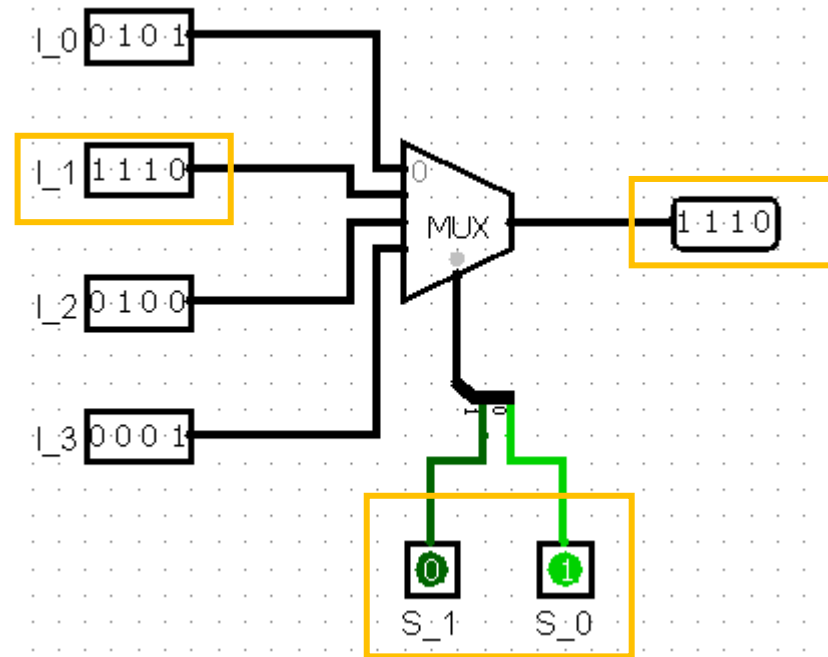

# Multiplexers

- 4x4 Multiplexer:

$S_1$	$S_0$	$M$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

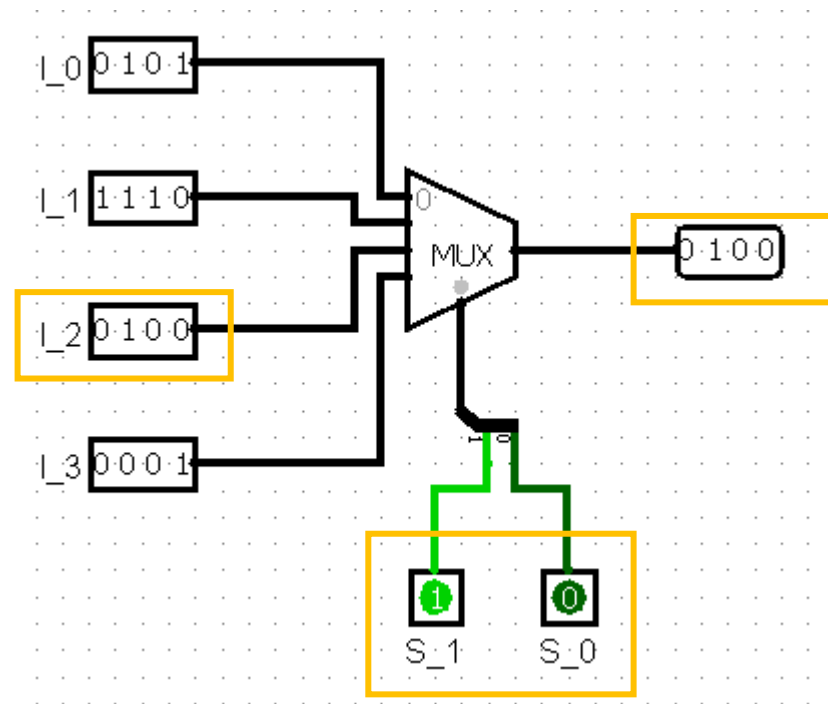




# Multiplexers

- 4x4 Multiplexer:


$S_1$	$S_0$	$M$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

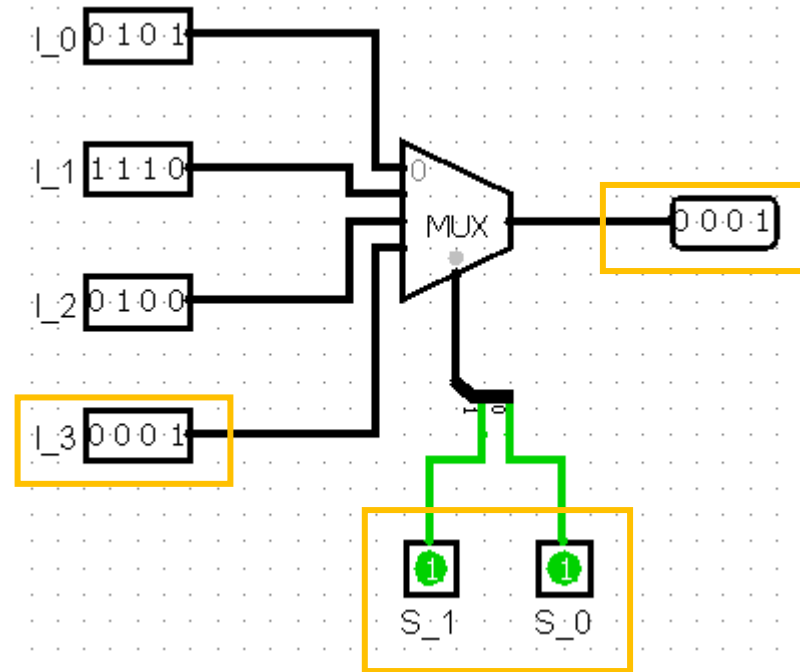

# Multiplexers

- 8x16 Multiplexer:


$S_2$	$S_1$	$S_0$	$M$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

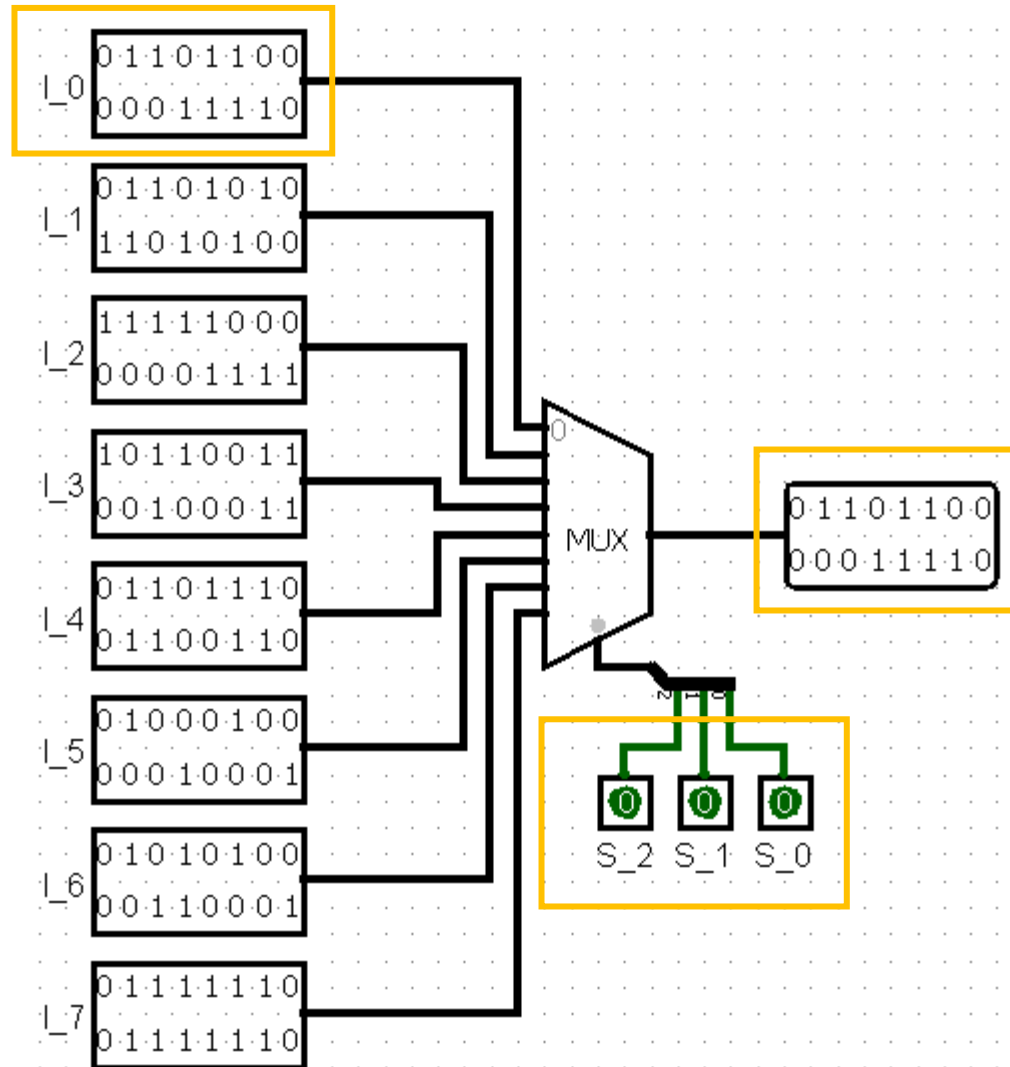

# Multiplexers

- 8x16 Multiplexer:

$S_2$	$S_1$	$S_0$	$M$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

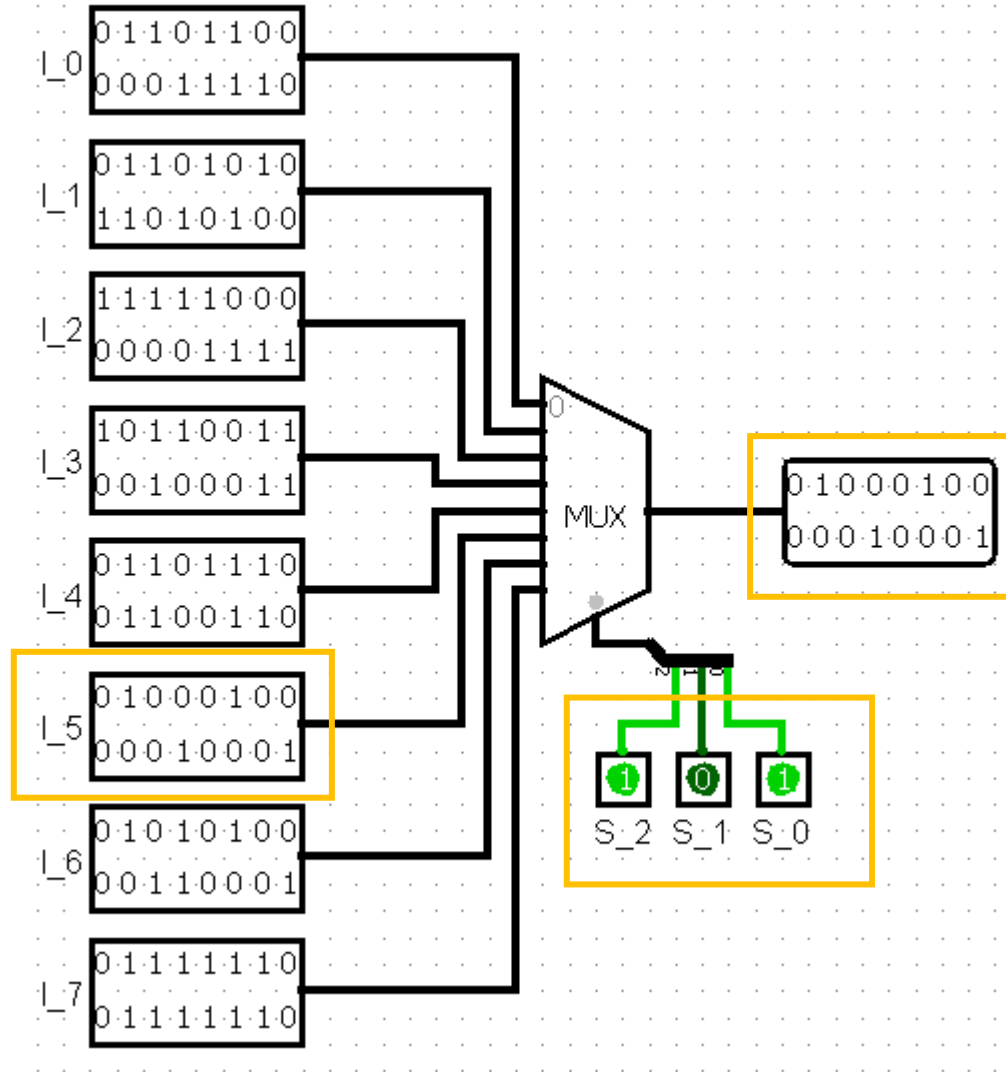

# Demultiplexers

- A demultiplexer (*DMX*) is a combinational logic circuit used to select the output from one input line
- A demultiplexer has 1 input pin,  $n$  select pins, and  $2^n$  output pins.

- The truth table for a 1x4 demultiplexer:
  - *I* represents the input pin
  - *S* represents the select pins (2)
  - *D* represents the output pins ( $4 = 2^2$ )

<i>S</i> <sub>1</sub>	<i>S</i> <sub>0</sub>	<i>D</i> <sub>3</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>0</sub>
0	0	0	0	0	<i>I</i>
0	1	0	0	<i>I</i>	0
1	0	0	<i>I</i>	0	0
1	1	<i>I</i>	0	0	0

# Demultiplexers

SOP Expressions:

$$D_0 = \bar{S}_1 \bar{S}_0 I$$

$$D_1 = \bar{S}_1 S_0 I$$


$$D_2 = S_1 \bar{S}_0 I$$

$$D_3 = S_1 S_0 I$$

$S_1$	$S_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	<b><math>I</math></b>
0	1	0	0	<b><math>I</math></b>	0
1	0	0	<b><math>I</math></b>	0	0
1	1	<b><math>I</math></b>	0	0	0

# Demultiplexers


- 1x4 Demultiplexer:

 

# Demultiplexers

- 1x4 Demultiplexer:


$S_1$	$S_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	$I$
0	1	0	0	$I$	0
1	0	0	$I$	0	0
1	1	$I$	0	0	0

 

# Demultiplexers

- 1x4 Demultiplexer:


$S_1$	$S_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	$I$
0	1	0	0	$I$	0
1	0	0	$I$	0	0
1	1	$I$	0	0	0

 



# Demultiplexers

- Abstracted 1x4 demultiplexer:

 

# Demultiplexers

- The truth table for a 1x8 multiplexer:
  - ***I*** represents the input pin
  - ***S*** represents the select pins (**3**)
  - ***D*** represents the output pins ( $8 = 2^3$ )

<b><i>S</i><sub>2</sub></b>	<b><i>S</i><sub>1</sub></b>	<b><i>S</i><sub>0</sub></b>	<b><i>D</i><sub>7</sub></b>	<b><i>D</i><sub>6</sub></b>	<b><i>D</i><sub>5</sub></b>	<b><i>D</i><sub>4</sub></b>	<b><i>D</i><sub>3</sub></b>	<b><i>D</i><sub>2</sub></b>	<b><i>D</i><sub>1</sub></b>	<b><i>D</i><sub>0</sub></b>
0	0	0	0	0	0	0	0	0	0	<b><i>I</i></b>
0	0	1	0	0	0	0	0	0	<b><i>I</i></b>	0
0	1	0	0	0	0	0	0	<b><i>I</i></b>	0	0
0	1	1	0	0	0	0	<b><i>I</i></b>	0	0	0
1	0	0	0	0	0	<b><i>I</i></b>	0	0	0	0
1	0	1	0	0	<b><i>I</i></b>	0	0	0	0	0
1	1	0	0	<b><i>I</i></b>	0	0	0	0	0	0
1	1	1	<b><i>I</i></b>	0	0	0	0	0	0	0

# Demultiplexers

SOP Expressions:

$$D_0 = \overline{S_2} \overline{S_1} \overline{S_0} I$$

$$D_1 = \overline{S_2} \overline{S_1} S_0 I$$

$$D_2 = \overline{S_2} S_1 \overline{S_0} I$$

$$D_3 = \overline{S_2} S_1 S_0 I$$

$$D_4 = S_2 \overline{S_1} \overline{S_0} I$$

$$D_5 = S_2 \overline{S_1} S_0 I$$


$$D_6 = S_2 S_1 \overline{S_0} I$$

$$D_7 = S_2 S_1 S_0 I$$

$S_2$	$S_1$	$S_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	<b><i>I</i></b>
0	0	1	0	0	0	0	0	0	<b><i>I</i></b>	0
0	1	0	0	0	0	0	0	<b><i>I</i></b>	0	0
0	1	1	0	0	0	0	<b><i>I</i></b>	0	0	0
1	0	0	0	0	0	<b><i>I</i></b>	0	0	0	0
1	0	1	0	0	<b><i>I</i></b>	0	0	0	0	0
1	1	0	0	<b><i>I</i></b>	0	0	0	0	0	0
1	1	1	<b><i>I</i></b>	0	0	0	0	0	0	0

# Demultiplexers


- 1x8 Demultiplexer:

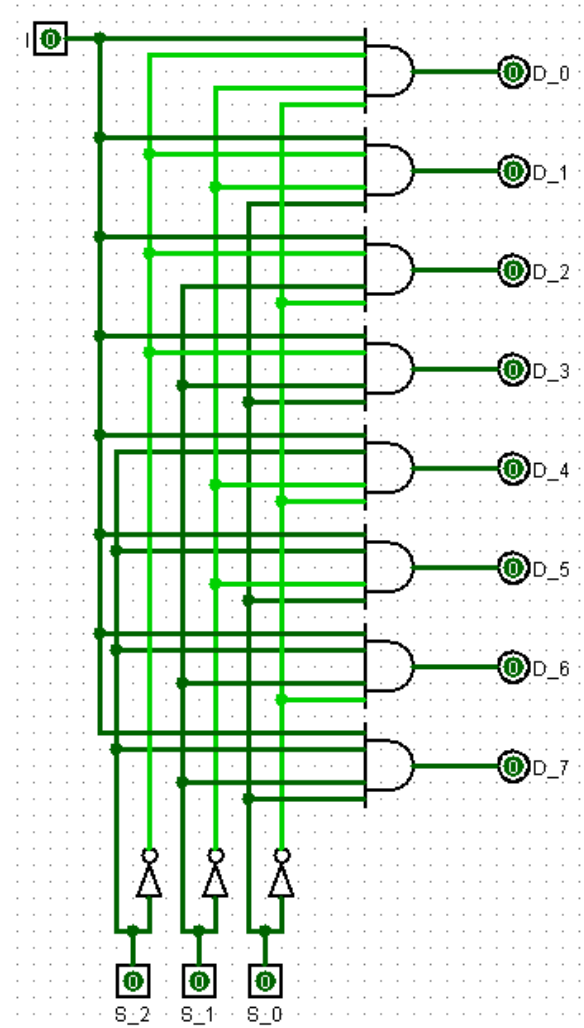

# Demultiplexers

- 1x8 Demultiplexer:


$S_2$	$S_1$	$S_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	$I$
0	0	1	0	0	0	0	0	0	$I$	0
<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b><math>I</math></b>	<b>0</b>	<b>0</b>
0	1	1	0	0	0	0	$I$	0	0	0
1	0	0	0	0	0	$I$	0	0	0	0
1	0	1	0	0	$I$	0	0	0	0	0
1	1	0	0	$I$	0	0	0	0	0	0
1	1	1	$I$	0	0	0	0	0	0	0

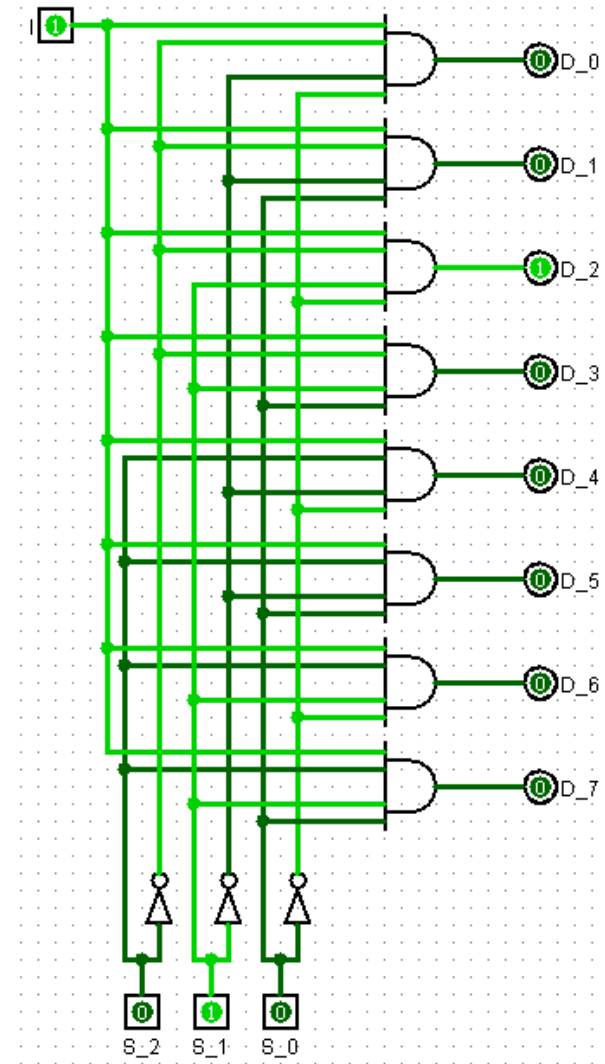

# Demultiplexers

- 1x8 Demultiplexer:

$S_2$	$S_1$	$S_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	$I$
0	0	1	0	0	0	0	0	0	$I$	0
0	1	0	0	0	0	0	0	$I$	0	0
0	1	1	0	0	0	0	$I$	0	0	0
1	0	0	0	0	0	$I$	0	0	0	0
1	0	1	0	0	$I$	0	0	0	0	0
1	1	0	0	$I$	0	0	0	0	0	0
1	1	1	$I$	0	0	0	0	0	0	0

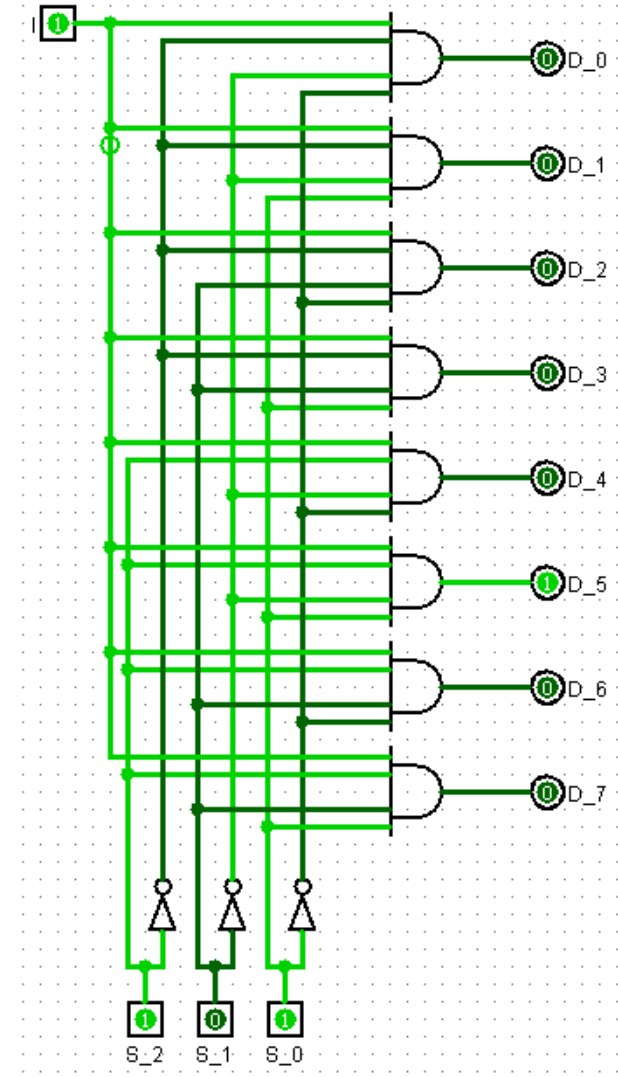

# Demultiplexers

- Abstracted 1x8 demultiplexer:

